



# NUZVID POLYTECHNIC

(Approved by AICTE, New Delhi & Affiliated to SBTET, AP)  
Venkatadripuram (V), Annavaram (Post), Nuzvid (M), Eluru (Dt), A.P-521201.



As per C-23

## AC CIRCUITS AND TRANSFORMERS & EE-303 Material



Prepared by  
**NAGARAJU DARELLI** M.Tech

Student Name : \_\_\_\_\_

PIN : \_\_\_\_\_

**Department of Electrical & Electronics Engineering**



## IMPORTANT NOTE

Q.No.	Target Date	Submission Date	Faculty signature
1			
2			
3			
4			
5			
6			
7			
8			
9			
10			
11			
12			
13			
14			
15			
16			
17			
18			
19			
20			
21			
22			
23			

Q.No.	Target Date	Submission Date	Faculty signature
24			
25			
26			
27			
28			
29			
30			
31			
32			
33			
34			
35			
36			
37			
38			
39			
40			
41			
42			
43			
44			
45			

[illegible]

[illegible]

**SHORT ANSWER QUESTIONS:-****1. Derive the relationship among Pole, Speed and Frequency.**

**Ans:** Let P= No. of poles

N= Rotor speed in rpm

F= Frequency in Hz

$$\text{No. of cycles per revolution} = \frac{P}{2}$$

$$\text{No. of revolution per second} = \frac{N}{60}$$

$$\begin{aligned}
 \text{Frequency} &= \frac{\text{No. of Cycles}}{\text{Second}} \\
 &= \frac{\text{No. of Cycles}}{\text{Revolution}} \times \frac{\text{No. of Revolution}}{\text{Second}} \\
 &= \frac{P}{2} \times \frac{N}{60}
 \end{aligned}$$

$$F = \frac{PN}{120} \text{ Hz}$$

**2. Define the terms Cycle, Time period and Frequency.**

**Ans:**

**Cycle:** One complete set of positive and negative values of an alternating quantity is known as “Cycle”.

**Time Period:** The time taken to complete one cycle of an alternating quantity is called “Time Period”.

**Frequency:** The no. of cycles per second by an alternating quantity is called “Frequency”.

**3. Define instantaneous value, maximum value, average value and RMS value.**

**Ans:**

**Instantaneous value:** The value of an alternating quantity at any instant of time is called “Instantaneous value”.

**Maximum value:** The height value attained by an alternating quantity is called “Maximum Value”.

**Average value:** It is defined as the arithmetic mean of all the values of over one complete cycle is called as “Average Value”.

**RMS value:** Is is defined as square root of the mean of the instantaneous values of an alternating quantity is called “RMS value”.

**4. Define form factor and peak factor.**

**Ans:**

**Form factor:** The ratio between RMS value to the average value of an alternating quantity is called “Form Factor”.

$$\text{Form Factor, } K_f = \frac{\text{RMS Value}}{\text{Average Value}}$$

**Peak Factor:** The ratio between Maximum value to the RMS value of an alternating quantity is known as “Peak Factor”.

$$\text{Peak Factor, } K_p = \frac{\text{Max. Value}}{\text{RMS Value}}$$

**5. Define phase and phase difference.**

**Ans: Phase:** The angle turned by an alternating quantity from a given instant is known as “Phase”.

**Phase Difference:** The angular displacement between two alternating quantities is called “Phase Difference”.

**6. Derive an expression for RMS value of half wave rectified sine wave.**

**Ans:** Let instantaneous value,  $v = V_m \sin \omega t$

$$\text{RMS value, } V_{\text{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2 d\omega t}$$

$$= \sqrt{\frac{1}{2\pi} \left( \int_0^{\pi} V_m^2 \sin^2(\omega t) d\omega t + \int_{\pi}^{2\pi} 0 d\omega t \right)}$$

Here  $\cos 2\theta = 1 - 2\sin^2(\theta)$

$$V_{\text{rms}} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{\pi} \left( \frac{1 - \cos 2\omega t}{2} \right) d\omega t}$$


$$= \sqrt{\frac{V_m^2}{4\pi} \left( [\omega t]_0^{\pi} - \left[ \frac{\sin 2\omega t}{2} \right]_0^{\pi} \right)}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \left( [\pi - 0] - \frac{\sin 2(\pi)}{2} + \frac{\sin 2(0)}{2} \right)}$$

$$= \sqrt{\frac{V_m^2}{4\pi} \pi}$$

$$= \sqrt{\frac{V_m^2}{2}}$$
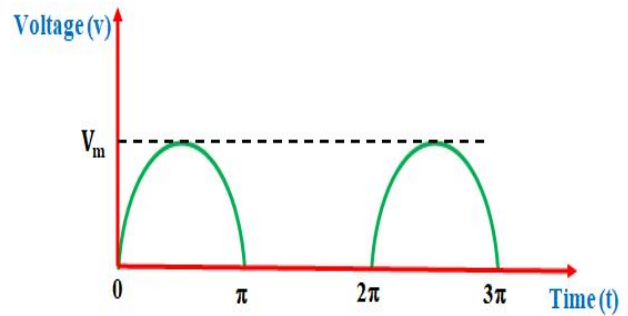
$$\boxed{V_{\text{rms}} = 0.5 V_m} \text{ Volts}$$



Half wave rectified sine wave

**7. Derive an expression average value of half wave rectified sine wave.**

**Ans:** Let instantaneous value,  $v = V_m \sin \omega t$

$$\text{Average value, } V_{\text{avg}} = \frac{1}{2\pi} \int_0^{2\pi} v d\omega t$$

$$= \frac{1}{2\pi} \left( \int_0^{\pi} V_m \sin \omega t d\omega t + \int_{\pi}^{2\pi} 0 d\omega t \right)$$


$$= \frac{V_m}{2\pi} [-\cos \omega t]_0^{\pi}$$

$$= \frac{V_m}{2\pi} (-\cos 2\pi + \cos 0)$$

$$= \frac{V_m}{2\pi} (1 + 1)$$

$$= \frac{V_m}{\pi}$$
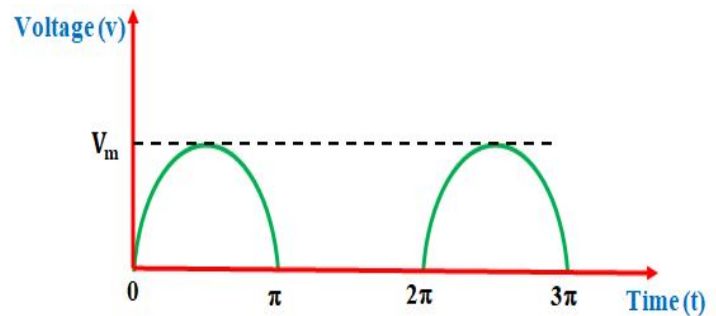
$$\boxed{V_{\text{avg}} = 0.31826 V_m} \text{ Volts}$$



Half wave rectified sine wave

**8. Derive an expression for RMS value of full wave rectified sine wave.**

**Ans:** Let instantaneous value,  $v = V_m \sin \omega t$

$$\text{RMS value, } V_{\text{rms}} = \sqrt{\frac{1}{\pi} \int_0^{\pi} v^2 d\omega t}$$

$$= \sqrt{\frac{1}{\pi} \int_0^{\pi} V_m^2 \sin^2(\omega t) d\omega t}$$

Here  $\cos 2\theta = 1 - 2\sin^2(\theta)$


$$= \sqrt{\frac{V_m^2}{\pi} \int_0^{\pi} \left( \frac{1 - \cos 2\omega t}{2} \right) d\omega t}$$

$$= \sqrt{\frac{V_m^2}{2\pi} \left( [\omega t]_0^{\pi} - \left[ \frac{\sin 2\omega t}{2} \right]_0^{\pi} \right)}$$

$$= \sqrt{\frac{V_m^2}{2\pi} (\pi - 0)}$$

$$= \sqrt{\frac{V_m^2}{2}}$$

$$V_{rms} = 0.707 V_m \text{ Volts}$$

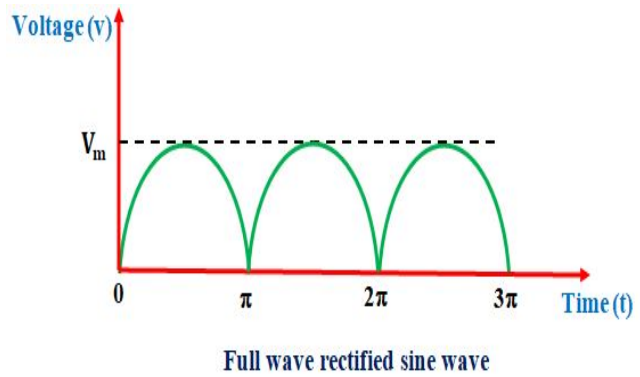

**9. Convert 3-j6 into polar form.**

**Ans:** 3-j6 is converted into polar form

$$|A| = \sqrt{(3)^2 + (-6)^2}$$

$$= \sqrt{45}$$

$$= 6.708$$

$$\theta = \tan^{-1} \left( \frac{-6}{3} \right)$$

$$= -63.43$$

$\therefore$

$$3-j6 = 6.708 \angle -63.43$$

**10. Convert  $100 \angle 45^\circ$  into rectangular form.**

**Ans:**  $100 \angle 45^\circ$  is converted into rectangular form

$$|A| \cos \theta + j |A| \sin \theta = 100 \cos 45 + j 100 \sin 45$$

$$= 70.71 + j70.71$$

$\therefore$

$$100 \angle 45^\circ = 70.71 + j70.71$$

**11. Define Q-factor of series resonance circuit.**

**Ans:** It is defined as the ratio between reactive power to the average power.

$$Q\text{-factor} = \frac{\text{Reactive Power}}{\text{Average Power}}$$

**12. Define conductance, susceptance & admittance and mention its units.**

**Ans:**

**Conductance:** The reciprocal of resistance is nothing but “Conductance”. The unit for conductance is mho.

$$\text{Conductance, } G = \frac{1}{R} \quad \Omega$$

**Susceptance:** The reciprocal of reactance is nothing but “Susceptance”. The unit for susceptance is mho.

$$\text{Susceptance, } B = \frac{1}{X} \quad \Omega$$

**Admittance:** The reciprocal of impedance is nothing but “Admittance”. The unit for admittance is mho.

$$\text{Admittance, } Y = \frac{1}{Z} \quad \Omega$$

13. Draw the impedance and power triangles.

Ans:

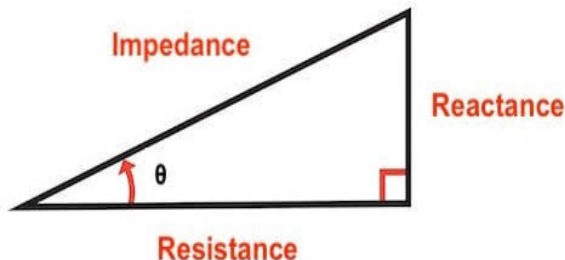


Fig.1 Impedance triangle for RL-Load

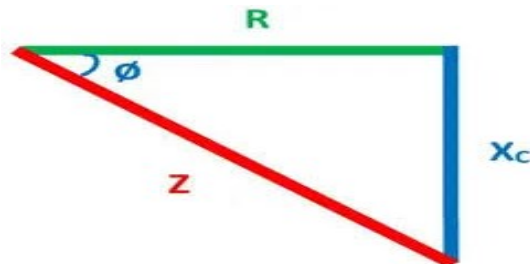


Fig.2 Impedance triangle for RC-Load

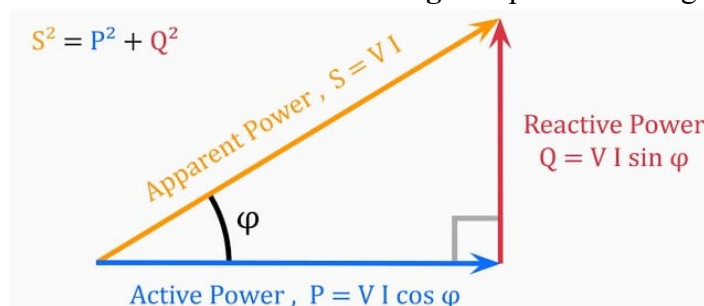


Fig.3 Power Triangle

14. Find the resonant frequency of RLC series circuit having resistance  $10\Omega$ , inductance  $20\text{mH}$  and capacitance  $100\mu\text{F}$ .

Ans:

**Given Data**

Resistance,  $R = 10\Omega$ ,

Inductance,  $L = 20\text{mH}$

Capacitance,  $C = 100\mu\text{F}$

$$\text{Resonant Frequency, } F_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{20 \times 10^{-3} \times 100 \times 10^{-6}}}$$

$$F_r = 112.53953 \text{ Hz}$$

**Require Data**

Resonant Frequency=?

15. Define active, reactive and apparent powers.

Ans:

**Active Power:** The power which is consumed by the consumer is called “Active Power”.

$$\text{Active Power, } P = VI \cos \phi \quad \text{Watts}$$

**Reactive Power:** The power which is flows from load to source is called “Reactive Power”.

$$\text{Reactive Power, } Q = VI \sin \phi \quad \text{VAR}$$

**Apparent Power:** The product of voltage and current is nothing but “Apparent Power”.

$$\text{Apparent Power, } S = VI \quad \text{VA}$$



16. What are the methods used to solve the parallel circuits.

Ans:

- ❖ Vector method
- ❖ Admittance method
- ❖ J-notation method

17. Define poly phase and phase sequence.

**Ans: Poly-Phase:** Poly means many and Phase means windings. Poly-phase system is a combination of two or more than two voltages having same magnitude and frequency but displaced from each other by an equal electrical angle.

**Phase Sequence:** The order in which the three phases reach their maximum value is known as “Phase Sequence”.

18. Define Line voltage, Phase voltage, Line current and Phase current.

Ans:

**Line Voltage:** The voltage between any two phases from 3- $\phi$  is called “Line Voltage”.

**Phase Voltage:** The voltage between any of the phase from 3- $\phi$  system to neutral is known as “Phase Voltage”

**Line Current:** The current flowing in the lines is called as “Line Current”.

**Phase Current:** The current flowing through the phase are called as “Phase Current”.

19. What are the advantages of 3- $\phi$  system over 1- $\phi$  system?

Ans:

- ❖ Greater output
- ❖ More efficient
- ❖ Self starting
- ❖ More reliable
- ❖ Better voltage regulation

20. Define transformer.

**Ans:** Transformer is a static device, which transfer the electrical energy from one circuit to other circuit without changing the frequency.


21. Distinguish between shell type and core type transformer.

Ans:

S.No.	Core Type Transformer	Shell Type Transformer
01	Construction is difficult	Easy construction
02	Rarely used	Widely used
03	Single magnetic circuit	Double magnetic circuit
04	Cylindrical concentric coils are used	Sandwiched disc type coils are used

22. Draw the approximate equivalent circuit of a transformer.

Ans:

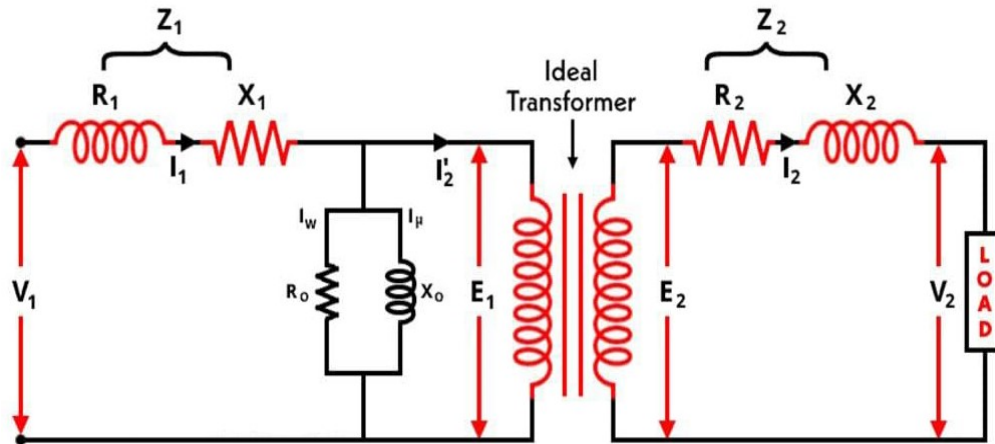

23. Define all-day efficiency.

Ans: It is defined as the ratio between energy outputs in 24Hours to the energy inputs in 24Hours.

$$\text{All-day efficiency, } \eta_{All-d} = \frac{\text{Energy output in KWH for 24 Hours}}{\text{Energy input in KWH for 24 Hours}}$$

24. List the various losses in a 1- $\phi$  transformer.

Ans: Total Losses  $\left\{ \begin{array}{l} 1. \text{Iron Losses} \left\{ \begin{array}{l} 1. \text{Hysteresis Losses} \\ 2. \text{Eddy Current Losse} \end{array} \right. \\ 2. \text{Copper Losses} \left\{ \begin{array}{l} 1. \text{Primary copper Losses} \\ 2. \text{Secondary copper Losses} \end{array} \right. \\ 3. \text{Stray Losses} \\ 4. \text{Dielectric Losses} \end{array} \right.$

25. State the reason for specifying the transformer ratings in KVA?

Ans: We know that iron loss in a transformer depends on voltage and copper losses depends on current. Therefore, the total losses in the transformer depends on Volt-Ampere and it is independent of load power factor. for this reason, the rating of a transformer is in KVA.

26. State the advantages of 3- $\phi$ transformers over 1- $\phi$  transformers.

Ans:

- ❖ It occupies less space
- ❖ Less weight
- ❖ Less cost
- ❖ More efficient.

27. State the conditions for parallel operation of 3- $\phi$  transformer.

Ans:

- ❖ Polarities of the two transformers must be same.
- ❖ The voltage ratings of the two transformers must be same.
- ❖ The percentage impedance must be same.
- ❖ Phase sequence must be the same.

**28. State the advantages of Auto transformer.****Ans:**

- ❖ Small size
- ❖ Less weight
- ❖ Low cost
- ❖ Less voltage drop
- ❖ Variable output

**29. State the applications of auto transformer.****Ans:**


- ❖ Voltage stabilizer
- ❖ Testing
- ❖ Speed control of fans
- ❖ Starter for motors.

**30. State the necessity of cooling of power transformer.**

**Ans:** In transformers losses are takes place in core and the windings. To keep down the temperature i.e; to dissipate the heat from the core and windings cooling system is necessary.

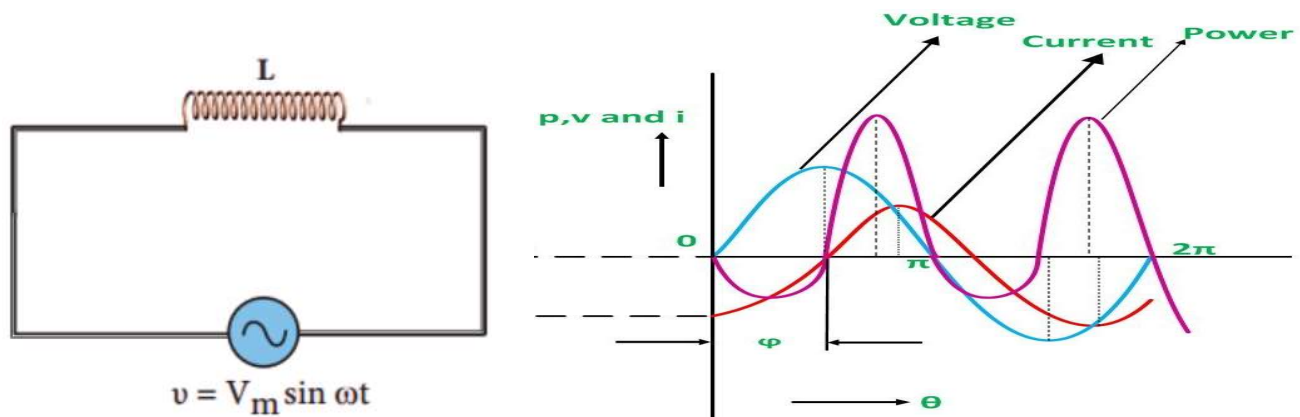**LONG ANSWER QUESTIONS****31. Show that the power consumed by a pure inductance is zero when AC supply is applied to Inductance.**

**Ans:** Consider a circuit containing a coil of pure inductance connected across an alternating voltage source.



Let an alternating voltage applied across the circuit,  $v = V_m \sin \omega t$

An alternating current 'I' flows through a pure inductive coil causes a back emf is induced in it.

$$e = -L \frac{di}{dt}$$

$$v = -e = - \left( -L \frac{di}{dt} \right)$$

$$v = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$di = \frac{1}{L} V_m \sin \omega t \, dt$$

Integrating above equation on both sides

$$\int di = \int \frac{1}{L} V_m \sin \omega t \, dt$$

$$i = \frac{V_m}{L} \left( \frac{-\cos \omega t}{\omega} \right)$$

$$i = \frac{-V_m}{\omega L} (\cos \omega t)$$

$$i = -I_{\max} \cos \omega t \quad \left[ \because I_{\max} = \frac{-V_m}{\omega L} \right]$$

The power consumed in the pure inductance at any instant is equal to the product of voltage and current at that instant.

$$\therefore \text{Instantaneous power, } p = vi = V_m \sin \omega t (-I_{\max} \cos \omega t)$$

$$= -V_m I_m \sin \omega t \cos \omega t$$

$$= \frac{-2 V_m I_m \sin \omega t \cos \omega t}{2}$$

$$= \frac{-V_m I_m}{2} \sin 2\omega t$$



$$\therefore \text{The power for whole cycle, } P = \int_0^{2\pi} \frac{-V_m I_m}{2} \sin 2\omega t \, dt$$

$$= \frac{-V_m I_m}{2} \int_0^{2\pi} \sin 2\omega t \, dt$$

$$\boxed{P = 0} \text{ Watts}$$

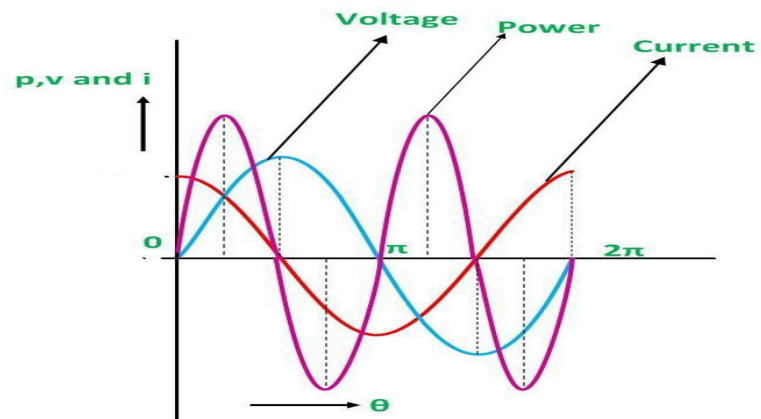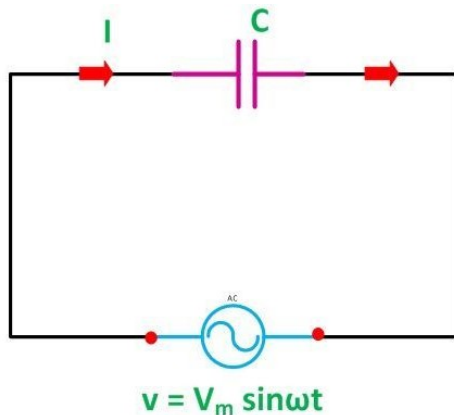**32. Show that the power consumed by a pure capacitance is zero when AC supply is applied to Capacitance.**

**Ans:** Let us consider a pure capacitance is connected across an AC supply.



Let instantaneous value,  $v = V_m \sin \omega t$

$$\text{Capacitance, } C = \frac{q}{v}$$

$$q = Cv = C V_m \sin \omega t$$

$$\text{We have } i = \frac{dq}{dt}$$

$$= \frac{d}{dt} (C V_m \sin \omega t)$$

$$= C V_m (\cos \omega t) \omega$$

$$= \omega C V_m (\cos \omega t)$$

$$= \frac{V_m}{1/\omega C} (\cos \omega t)$$

$$i = I_{\max} \cos \omega t$$

$$\left[ \because I_{\max} = \frac{V_m}{1/\omega C} \right]$$

Instantaneous power,  $p = vi$

$$= V_m \sin \omega t I_m \cos \omega t$$

$$= \frac{V_m I_m}{2} 2 \sin \omega t \cos \omega t$$

$$= \frac{V_m I_m}{2} \sin 2\omega t$$

$$\therefore \text{The power for whole cycle, } P = \int_0^{2\pi} \frac{V_m I_m}{2} \sin 2\omega t \, dt$$

$$= \frac{V_m I_m}{2} \int_0^{2\pi} \sin 2\omega t \, dt$$

$$P = 0 \text{ Watts}$$

**33. A resistance of  $10\Omega$  and inductance  $0.1\text{H}$  are connected in series across a supply of  $220\text{V}, 50\text{Hz}$ . Find (a). Impedance (b). Current flowing (c). Power factor and (d). Phase angle.**

**Ans: Given Data**

Resistance,  $R = 10\Omega$

Inductance,  $L = 0.1\text{H}$

Voltage,  $V = 220\text{Volts}$

Frequency,  $F = 50\text{Hz}$

**Require Data**

Impedance,  $Z = ?$

Current,  $I = ?$

Power factor = ?

Phase angle = ?

(i). Impedance,  $Z = \sqrt{R^2 + X_L^2}$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.1$$

$$X_L = 31.41592\Omega$$

then  $Z = \sqrt{(10)^2 + (31.41592)^2}$

$$Z = 32.96290\Omega$$

(ii). Current,  $I = \frac{V}{Z} = \frac{220}{32.96290}$


$$I = 6.67416 \text{ Amps}$$

(iii). Power Factor,  $\cos \phi = \frac{R}{Z} = \frac{10}{32.96290}$

$$\cos \phi = 0.30337 \text{ lag}$$

(iv). Phase angle,  $\phi = \cos^{-1}(0.30337)$

$$\phi = 72.34^\circ$$

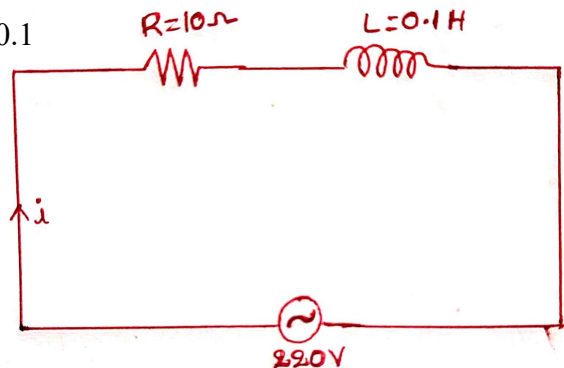

**34. A capacitor of  $50\mu\text{F}$  is connected in series with a resistor of  $100\Omega$ . This combination is connected across a  $230\text{V}, 50\text{Hz}$  AC supply. Calculate impedance, Current, Power factor, Active power and reactive power.**

**Ans: Given Data**

Resistance,  $R = 100\Omega$

Capacitor,  $C = 50\mu\text{F}$

Voltage,  $V = 230\text{Volts}$

**Require Data**

$Z = ?$

$I = ?$

$\cos \phi = ?$

Frequency,  $F = 50\text{Hz}$  $P = ?$  $Q = ?$ 

(i). Impedance,  $Z = \sqrt{R^2 + X_C^2}$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}}$$

$$X_C = 63.66197 \Omega$$

$$Z = \sqrt{(100)^2 + (63.66197)^2}$$

$$Z = 118.5447 \Omega$$

(ii). Current,  $I = \frac{V}{Z} = \frac{230}{118.5447}$

$$I = 1.94019 \text{ Amps}$$

(iii). Power Factor,  $\cos \phi = \frac{R}{Z} = \frac{100}{118.5447}$

$$\cos \phi = 0.84356 \text{ lead}$$

$$\phi = \cos^{-1}(0.84356)$$


$$\phi = 32.48^\circ$$

(iv). Active power,  $P = VI \cos \phi = 230 \times 1.94019 \times 0.84356$

$$P = 376.43335 \text{ Watts}$$

(v). Reactive power,  $Q = VI \sin \phi = 230 \times 1.94019 \times \sin(32.48)$

$$Q = 239.63517 \text{ VAR}$$

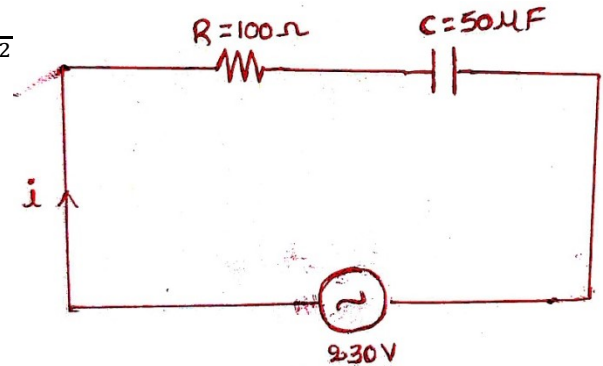

35. A resistance of  $12\Omega$ , an inductance of  $0.15\text{H}$  and a capacitance of  $100\mu\text{F}$  are connected in series across a  $100\text{V}$ ,  $50\text{Hz}$  supply. Calculate impedance, Current, Power factor and Power consumed.

Ans:

Given DataResistance,  $R = 12 \Omega$ Inductance,  $L = 0.15\text{H}$ Capacitor,  $C = 100\mu\text{F}$ Voltage,  $V = 100\text{Volts}$ Frequency,  $F = 50\text{Hz}$ 

Impedance,  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.15$$

$$X_L = 47.12388 \Omega$$

$$X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}}$$

$$X_C = 31.83098 \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{12^2 + (47.12388 - 31.83098)^2}$$

$$Z = 19.43895 \Omega$$

Current,  $I = \frac{V}{Z} = \frac{100}{19.43895}$


Require Data

$$Z = ?$$

$$I = ?$$

$$\cos \phi = ?$$

$$P = ?$$

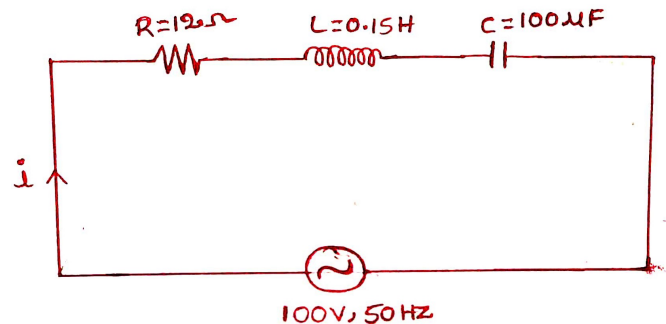

$$I = 5.14431 \text{ Amps}$$

$$\text{Power factor, } \cos \phi = \frac{R}{Z} = \frac{12}{19.43895}$$

$$\cos \phi = 0.6176 \text{ lag}$$

$$\text{Power, } P = VI \cos \phi = 100 \times 5.14431 \times 0.6176$$

$$P = 317.56653 \text{ Watts}$$

### 36. Define series resonance and derive an expression for resonance frequency.

**Ans:** In the series RLC circuit the applied voltage and resultant current are in-phase. Then this circuit is known as "Series Resonance".

At resonance condition

$$X_L - X_C = 0$$

$$X_L = X_C$$

$$\omega_r L = \frac{1}{\omega_r C}$$


$$\omega_r^2 = \frac{1}{LC}$$

$$\omega_r = \sqrt{\frac{1}{LC}}$$

$$2\pi f_r = \frac{1}{\sqrt{LC}}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$
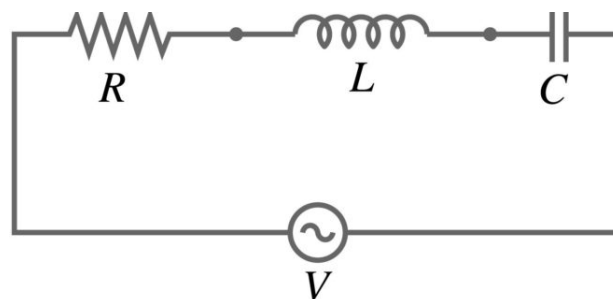
$$\therefore \text{Resonance frequency, } f_r = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$



### 37. Two impedances $Z_1 = 6+j6$ and $Z_2 = 6-j6$ are connected in parallel. Calculate the total (i).Conductance (ii).Susceptance (iii).Admittance (iv).Current taken from the supply and its PF.

If the supply voltage is 200V, 50Hz.

**Ans:** Given Data

$$Z_1 = 6+j6$$

$$Z_2 = 6-j6$$

$$V = 200 \text{ Volts}$$

$$F = 50 \text{ Hz}$$

Admittance for branch-1,

$$Y_1 = \frac{1}{Z_1} = \frac{1}{6+j6}$$

$$Y_1 = 0.08333 - j0.08333 \text{ } \Omega$$

Admittance for branch-2,

$$Y_2 = \frac{1}{Z_2} = \frac{1}{6-j6}$$

$$Y_2 = 0.08333 + j0.08333 \text{ } \Omega$$


Require Data

$$G = ?$$

$$B = ?$$

$$Y = ?$$

$$I = ?$$

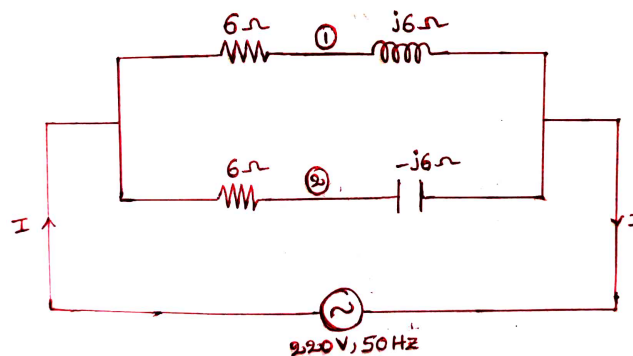

Total admittance,  $Y = Y_1 + Y_2 = 0.08333 - j0.0833 + 0.08333 + j0.08333$

$$Y = 0.16666 \text{ } \Omega$$

Current,  $I = VY = 200 \times 0.16666$

$$I = 33.332 \text{ Amps}$$

Conductance,  $G = 0.16666 \text{ } \Omega$

Susceptance,  $B = 0 \text{ } \Omega$

Phase angle,  $\phi = \tan^{-1} \left( \frac{B}{G} \right) = \tan^{-1} \left( \frac{0}{0.16666} \right)$



$$\phi = 0^\circ$$

Power factor,  $\cos \phi = \cos(0)$

$$\cos \phi = 1 (\text{Unity})$$

**38. Derive an expression for the line voltage and phase voltage in Star connected system.**

**Ans:**

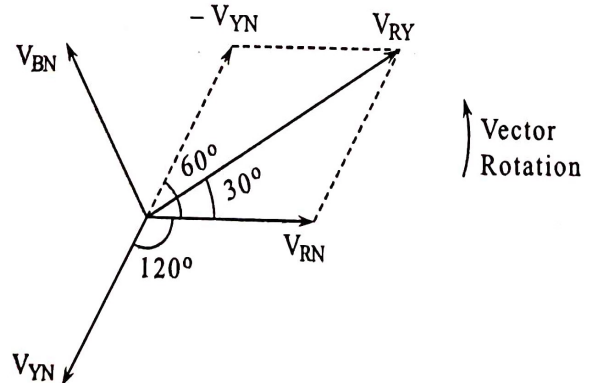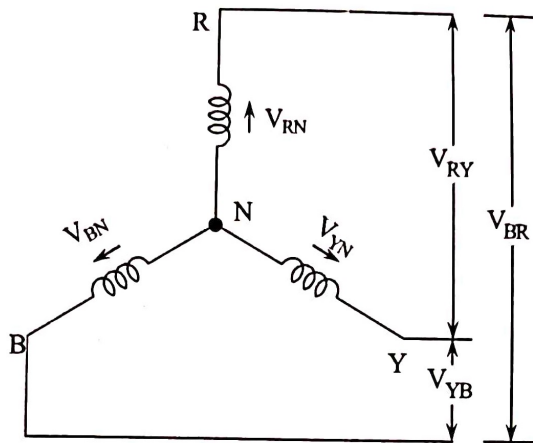

From the above fig.

$V_{RN}$ ,  $V_{YN}$  &  $V_{BN}$  are the phase voltages i.e;  $V_{RN} = V_{YN} = V_{BN} = V_{ph}$

$V_{RY}$ ,  $V_{YB}$  &  $V_{BR}$  are the line voltages i.e;  $V_{RY} = V_{YB} = V_{BR} = V_L$

The voltage between R-phase and Y-Phase is

$$V_{RY} = V_{RN} - V_{NY}$$

$$V_{RY} = V_{RN} - V_{YN}$$

Similarly  $V_{YB} = V_{YN} - V_{BN}$

$$V_{BR} = V_{BN} - V_{RN}$$

From the vector diagram, the voltage between R-Phase and Y-Phase is

$$V_{RY} = \sqrt{V_{RN}^2 + V_{YN}^2 + 2V_{RN}V_{YN} \cos 60^\circ}$$



$$V_L = \sqrt{V_{Ph}^2 + V_{Ph}^2 + 2V_{Ph}V_{Ph} \times \frac{1}{2}}$$

$$= \sqrt{3V_{Ph}^2}$$

$$V_L = \sqrt{3} V_{Ph} \text{ Volts}$$

In the 3-Ø star connected system, the line voltage is equal to  $\sqrt{3}$  times to the phase voltage i.e;  
 $V_L = \sqrt{3} V_{Ph}$  and the line current is equal to phase current i.e;  $I_L = I_{ph}$ .

**39. Three coils each having a resistance of  $20\Omega$  and an inductive reactance of  $15\Omega$  are connected in star to 400V, 3-Ø, 50Hz supply. Calculate line current, power factor and power supplied.**

**Ans:**      Given Data

$$R_{ph} = 20\Omega$$

$$X_L = 15\Omega$$

$$V_L = 400\text{Volts}$$

$$F = 50 \text{ Hz, 3-Ø star}$$

Require Data

$$I_L = ?$$

$$\cos \phi = ?$$

$$P = ?$$

$$\text{Impedance per phase, } Z_{ph} = \sqrt{(20)^2 + (15)^2}$$

$$Z_{ph} = 25 \Omega$$

$$\text{Phase voltage, } V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{400}{\sqrt{3}}$$

$$V_{ph} = 230.94 \text{ Volts}$$

$$\text{Phase current, } I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{230.94}{25}$$

$$I_{ph} = 9.2376 \text{ Amps}$$

$$\text{Line current, } I_L = I_{ph} = 9.2376 \text{ Amps}$$

$$\text{Power factor, } \cos \phi = \frac{R}{Z} = \frac{20}{25}$$

$$\cos \phi = 0.8 \text{ lag}$$

$$\text{Power supplied, } P = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} \times 400 \times 9.2376 \times 0.8$$

$$P = 5119.99761 \text{ Watts}$$

$$P = 5.11999 \text{ KW}$$

**40. A balanced 3-Ø star connected load of 100KW taken a lagging current of 75Amps with a line voltage of 1000Volts, 50Hz. Find the circuit constant of load per phase.**

**Ans:**

Given Data

$$P = 100\text{KW}$$

$$I_L = 75\text{Amps}$$

$$V_L = 1000\text{Volts}$$

$$F = 50 \text{ Hz, 3-Ø star}$$

Require Data

$$R = ?$$

$$L = ?$$

$$X_L = ?$$

$$Z = ?$$

$$\text{Phase voltage, } V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{1000}{\sqrt{3}}$$

$$V_{ph} = 577.35026 \text{ Volts}$$

$$I_L = I_{ph} = 75 \text{ Amps}$$

$$Z_{ph} = \frac{V_{ph}}{I_{ph}} = \frac{577.35026}{75}$$

$$\boxed{Z_{ph} = 7.698} \Omega$$

$$\text{Power supplied, } P = \sqrt{3} V_L I_L \cos \phi$$

$$\cos \phi = \frac{P}{\sqrt{3} V_L I_L} = \frac{100 \times 10^3}{\sqrt{3} \times 1000 \times 75}$$

$$\cos \phi = 0.7698 \text{ lag}$$

$$\text{Resistance, } R = Z \cos \phi = 7.698 \times 0.7698$$

$$\left[ \because \text{pf, } \cos \phi = \frac{R}{Z} \right]$$

$$\boxed{R = 5.92592} \Omega$$

$$\text{Reactance, } X_L = \sqrt{Z^2 - R^2} = \sqrt{(7.698)^2 - (5.92592)^2}$$

$$\boxed{X_L = 4.91351} \Omega$$


$$\text{Inductance, } L = \frac{X_L}{2\pi f} = \frac{4.91351}{2\pi \times 50}$$

$$= 0.01564 \text{ H}$$


$$\boxed{L = 15.64} \text{ mH}$$

41. Derive an expression for the line current and phase current in delta connected system.

Ans:

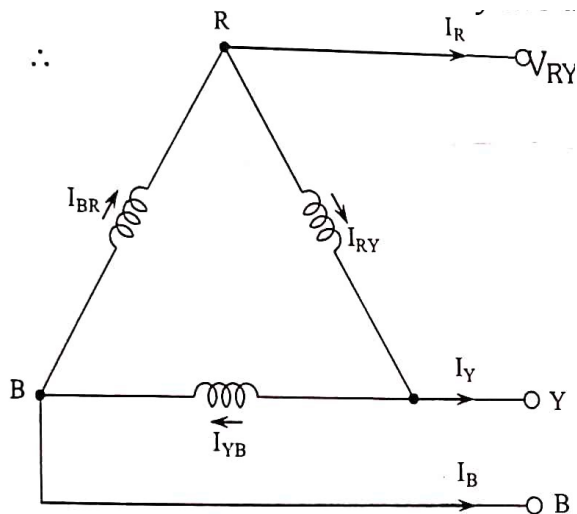

$$V_L = V_{Ph}$$

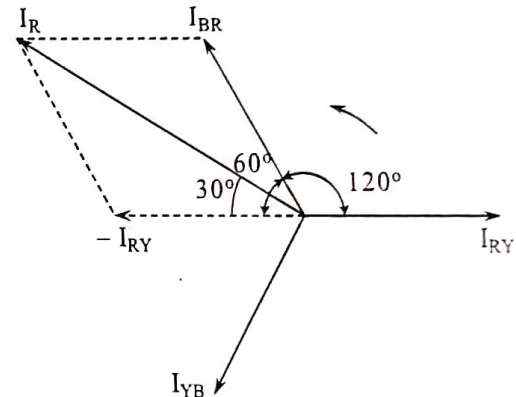

From the above fig.

$I_{RY}$ ,  $I_{YB}$  &  $I_{BR}$  are the phase currents i.e;  $I_{RY} = I_{YB} = I_{BR} = I_{ph}$

$I_R$ ,  $I_Y$  &  $I_B$  are the line currents i.e;  $I_R = I_Y = I_B = I_L$

From the vector diagram, the line current,

$$I_R = I_{BR} - I_{RY}$$

$$I_Y = I_{RY} - I_{YB}$$

$$I_B = I_{YB} - I_{BR}$$

$$\text{Line current, } I_R = \sqrt{I_{BR}^2 + I_{RY}^2 + 2I_{BR}I_{RY} \cos 60^\circ}$$

$$I_L = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}I_{ph} \times \frac{1}{2}}$$

$$= \sqrt{3I_{Ph}^2}$$

$$I_L = \sqrt{3} I_{Ph} \text{ Amps}$$

In the 3-Ø delta connected system, the line current is equal to  $\sqrt{3}$  times to the phase current i.e;  
 $I_L = \sqrt{3} I_{Ph}$  and the line voltage is equal to phase voltage i.e;  $V_L = V_{ph}$

**42. Three coils each having a resistance of  $10\Omega$  and an inductance of  $0.02H$  are connected (i) In star connection (ii).Delta connection to a 3-Ø, 50Hz. The line voltage being 500volts. Calculate the line current and power taken from the supply.**

**Ans:**

**Given Data**

$$R = 10\Omega$$

$$L = 0.02H$$

$$V_L = 500\text{Volts}$$

$$F = 50\text{Hz}$$

**Require Data**

$I_L$  & P for star & delta

**For star connection:-**

$$V_{ph} = \frac{V_L}{\sqrt{3}} = \frac{500}{\sqrt{3}} = 288.67513 \text{ Volts}$$

$$I_{Ph} = \frac{V_{ph}}{Z_{ph}}$$

$$X_L = 2\pi fL = 2\pi \times 50 \times 0.02$$

$$X_L = 6.28318 \Omega$$

$$Z_{ph} = \sqrt{R_{ph}^2 + X_L^2} = \sqrt{(10)^2 + (6.28318)^2}$$

$$= 11.77828 \Omega$$

$$\text{Then } I_{Ph} = \frac{288.67513}{11.77828}$$

$$I_{Ph} = 24.5091 \text{ Amps}$$

$$\text{Line current, } I_L = I_{Ph} = 24.5091 \text{ Amps}$$

$$\text{Power supplied, } P = \sqrt{3} V_L I_L \cos \phi$$

$$\text{Power factor, } \cos \phi = \frac{R}{Z} = \frac{10}{11.77828}$$

$$\cos \phi = 0.84902 \text{ lag}$$

$$P = \sqrt{3} \times 500 \times 24.5091 \times 0.84902$$

$$P = 18.02088 \text{ KW}$$

**For Delta connection:-**

$$V_L = V_{Ph} = 500 \text{ volts}$$

$$I_L = \sqrt{3} I_{Ph}$$

$$I_{Ph} = \frac{V_{Ph}}{Z_{Ph}} = \frac{500}{11.77828}$$

$$I_{Ph} = 42.45102 \text{ Amps}$$

$$\text{Then Line current, } I_L = \sqrt{3} \times 42.45102$$

$$I_L = 73.52732 \text{ Amps}$$

$$\text{Power, } P = \sqrt{3} \times 500 \times 73.52732 \times 0.84902$$

$$= 54062.64495 \text{ Watts}$$

$$P = 54.06264 \text{ KW}$$

#### 43. Derive the relationship between power in star and delta connected system.

**Ans:** For a star connected load,  $V_L = \sqrt{3} V_{Ph}$

$$I_{Ph} = \frac{V_{Ph}}{Z_{Ph}}$$

$$= \frac{V_L}{\sqrt{3} \times Z_{Ph}}$$

$$I_L = I_{Ph} = \frac{V_L}{\sqrt{3} \times Z_{Ph}}$$

$$\text{Now power in star connected load, } P_Y = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} V_L \frac{V_L}{\sqrt{3} \times Z_{Ph}} \cos \phi$$

$$P_Y = \frac{V_L^2}{Z_{ph}} \cos \phi \quad \text{-----} \rightarrow 1$$

For a delta connected load,  $V_L = V_{Ph}$

$$I_{Ph} = \frac{V_{Ph}}{Z_{Ph}}$$

$$= \frac{V_L}{Z_{Ph}}$$

$$I_L = \sqrt{3} I_{Ph} = \frac{\sqrt{3} V_L}{Z_{Ph}}$$

$$\text{Now power in star connected load, } P_\Delta = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} V_L \frac{\sqrt{3} V_L}{Z_{Ph}} \cos \phi$$

$$= 3 \frac{V_L^2}{Z_{ph}} \cos \phi \quad \text{-----} \rightarrow 2$$

From eq'n 1&2



$$P_\Delta = 3 P_Y$$

$$P_Y = \frac{1}{3} P_\Delta$$

**Note:** The power consumed by a balanced star connected load is one-third of that in case of a delta connected load.

44. Reduce the equation for power factor of the load using two watt-meter method.

Ans:

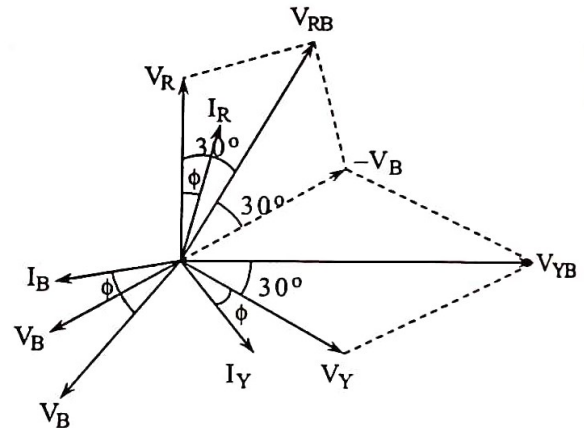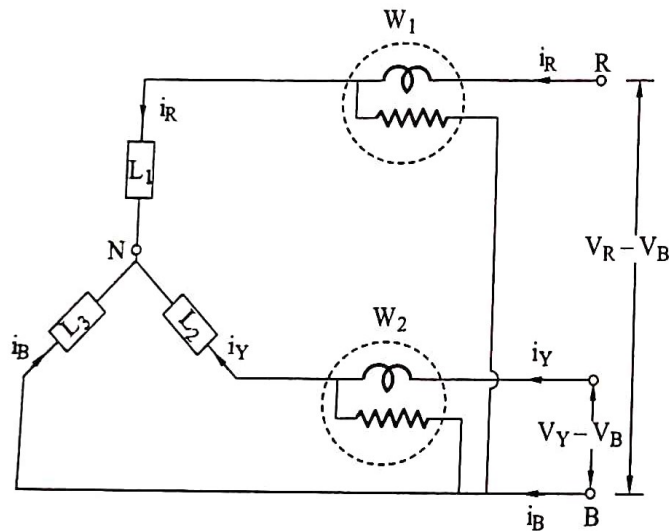

$$\text{Watt-meter, } W_1 = V_L I_L \cos(30 - \phi) \quad \text{-----} \rightarrow 1$$

$$\text{Watt-meter, } W_2 = V_L I_L \cos(30 + \phi) \quad \text{-----} \rightarrow 2$$

Adding eq'n 1 & 2

$$\begin{aligned} W_1 + W_2 &= V_L I_L \cos(30 - \phi) + V_L I_L \cos(30 + \phi) \\ &= V_L I_L (\cos(30 - \phi) + \cos(30 + \phi)) \\ &= V_L I_L (2 \cos 30^\circ \cos \phi) \\ &= V_L I_L \left( 2 \frac{\sqrt{3}}{2} \cos \phi \right) \end{aligned}$$

$$W_1 + W_2 = \sqrt{3} V_L I_L \cos \phi \quad \text{-----} \rightarrow 3$$

Subtract eq'n 1 & 2

$$\begin{aligned} W_1 - W_2 &= V_L I_L \cos(30 - \phi) - V_L I_L \cos(30 + \phi) \\ &= V_L I_L (\cos(30 - \phi) - \cos(30 + \phi)) \\ &= V_L I_L (2 \sin 30^\circ \sin \phi) \\ &= V_L I_L \left( 2 \frac{1}{2} \sin \phi \right) \end{aligned}$$

$$W_1 - W_2 = V_L I_L \sin \phi \quad \text{-----} \rightarrow 4$$

Divide  $\frac{\text{Eq'n 4}}{\text{Eq'n 3}}$

$$\begin{aligned} \frac{W_1 - W_2}{W_1 + W_2} &= \frac{V_L I_L \sin \phi}{\sqrt{3} V_L I_L \cos \phi} \\ &= \frac{1}{\sqrt{3}} \tan \phi \end{aligned}$$

$$\tan \phi = \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right)$$

$$\phi = \tan^{-1} \left( \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right)$$

$$\therefore \text{ Power factor, } \cos \phi = \cos \left( \tan^{-1} \left( \sqrt{3} \left( \frac{W_1 - W_2}{W_1 + W_2} \right) \right) \right)$$

45. Two watt-meters when connected to a 3-Ø, 400Volts, 50Hz motor shown a total load of 20KW. The power factor is 0.45lagging. What is the reading of each watt-meter.

Ans:

Given Data

$$V_L = 400\text{Volts}$$

$$f = 50\text{Hz}$$

$$P = 20\text{KW}$$

$$\cos \phi = 0.45$$

We know that,  $\cos \phi = 0.45$

$$\phi = \cos^{-1}(0.45)$$

$$\phi = 63.26'$$

$$V_L I_L = \frac{P}{\sqrt{3} \cos \phi}$$

$$= \frac{20 \times 10^3}{\sqrt{3} \times 0.45}$$

$$V_L I_L = 25660.01196 \quad \text{VA}$$

$$\text{Watt-meter, } W_1 = V_L I_L \cos(30 - \phi)$$

$$= 25660.01196 \times \cos(30 - 63.26)$$

$$W_1 = 21.45665 \text{ KW}$$

$$\text{Watt-meter, } W_2 = V_L I_L \cos(30 + \phi)$$

$$= 25660.01196 \times \cos(30 + 63.26)$$

$$W_2 = -1.45 \text{ KW}$$

*\*\*\* All the very best \*\*\**