



C23-EE-106

23061

BOARD DIPLOMA EXAMINATION, (C-23)

OCTOBER/NOVEMBER—2025

DEEE – FIRST YEAR EXAMINATION

BASIC ELECTRICAL TECHNOLOGY

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. State Ohm's law. 3
2. A charge equal to 5.6 Coulombs is crossing over a point in a circuit in 2.8 sec. Find the current flowing in the circuit. 3
3. Define temperature coefficient of resistance and state its SI units. 2+1
4. Write any three differences between active and passive circuits. 3
5. Define electrical power and mention its SI units. 2+1
6. State Joule's law of electrical heating. 3
7. An electric heater draws a current of 12 A from a supply of 230 V. If the load is connected for 10 hours, find the energy consumed in kWh. 3


8. Define ideal current source and draw its characteristics. 2+1
9. State superposition theorem. 3
10. What is the need of network theorems? 3

PART—B


10×5=50

Instructions : (1) Answer *any five* questions.
 (2) Each question carries **ten** marks.
 (3) Answers should be comprehensive and the criteria for valuation is the content but not the length of the answer.

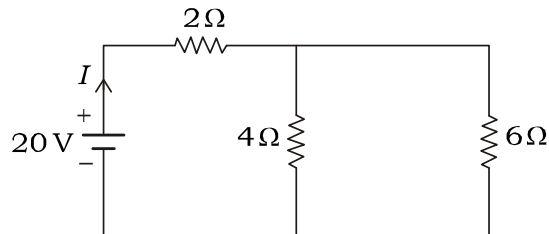11. (a) Derive the expression for resistance at any temperature, i.e.
 $R_t = R_0 (1 + \alpha_0 t)$
- (b) A rectangular carbon block has dimensions $1\text{ cm} \times 1\text{ cm} \times 50\text{ cm}$. If the resistivity of carbon is $3.5 \times 10^{-5} \Omega\text{-m}$, find the resistance between
 (i) opposite ends (ii) opposite rectangular faces. 4+6
12. Find the currents flowing through 4Ω and 6Ω resistances by using current division rule in the circuit shown below : 10



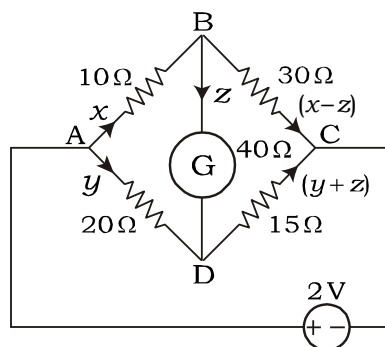13. Calculate the current flowing through the galvanometer in the following Wheatstone bridge network : 10




- 14.** Calculate the monthly bill of a household consumer for the following loads in a month of 30 days if the cost of energy per unit is ₹3.50 10
- (a) 4 lamps of 100 W each working for 6 hours a day
- (b) 3 fans of 60 W each working for 10 hours a day
- (c) An immersion heater of 2000 W is working for 1 hour a day
- (d) An electric iron of 1000 W working for 1 hour a day


- 15.** An electric kettle rated at 1 kW, takes 7.5 minutes to bring 1 kg of water at 15°C to boiling point. Find (a) efficiency of the kettle (b) current taken if the supply voltage is 230 V. 10

- 16.** Develop the transformation formulae for converting Delta configuration into Star configuration. 10

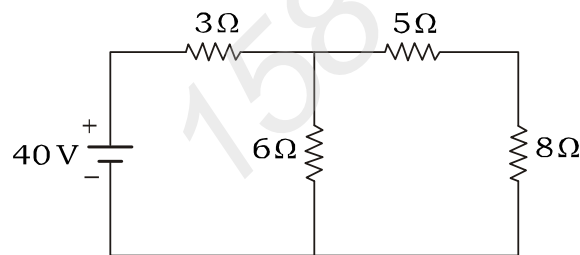- 17.** Using Thevenin's theorem, find the current through 8 Ω resistance in the circuit shown below : 10



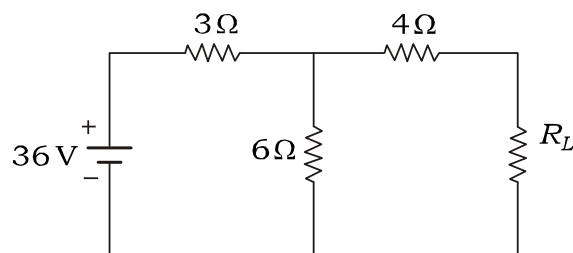- 18.** Find the value of R_L for which maximum power will be absorbed in it and determine the maximum power in the circuit shown below : 10



★ ★ ★