



**C23-EE-303**

**23136**

**BOARD DIPLOMA EXAMINATION, (C-23)  
OCTOBER/NOVEMBER—2024  
DEEE – THIRD SEMESTER EXAMINATION  
AC CIRCUITS AND TRANSFORMERS**

*Time : 3 Hours ]*

*[ Total Marks : 80*

**PART—A**

3×10=30

- Instructions :** (1) Answer **all** questions.  
(2) Each question carries **three** marks.  
(3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. Derive the relation between number of poles, speed and frequency.
2. A sinusoidal wave is represented by  $i = 42\sin 628t$ . Determine the  
(a) R.M.S value (b) Average value (c) Frequency.
3. Perform the following operations and express the result in polar form :  
(a)  $A \times B$  (b)  $A/B$ , where  $A = (6 + j8)$ ,  $B = (3 - j4)$
4. The voltage across a  $1\mu\text{F}$  capacitor is given by  $v = 170\sin 400t$ . What is sinusoidal expression for current?
5. Write the equations for instantaneous voltage and current in R-L series circuit.
6. Write the relation between line voltage and a phase voltage in a 3-phase star connection and delta connection.

7. Three similar resistances are connected in star across three-phase supply. Write the equation for power.
8. Write the difference between core and shell type transformers.
9. Draw the vector diagram of a transformer on no load and mention all the parameters.
10. What are the applications of auto transformer?

**PART—B**

10×5=50

**Instructions :** (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

11. A  $15\ \Omega$  resistor and  $200\ \mu\text{F}$  capacitor are connected in series to a 60V sinusoidal supply. The current of 3 A is flowing. Calculate (a) Voltage across capacitor and resistor, (b) the supply frequency and (c) phase angle between voltage and current.
12. (a) Derive expression for resonance frequency  $f_r$  in a RLC series circuit.  
(b) Derive an expression for Q-factor of RLC series circuit.
13. Derive the formula for calculating  $3\ \phi$  power and power factor from the readings of two wattmeters for measuring power in 3-phase circuit.
14. A balanced 3-phase star connected load 150 kW takes a leading current 100 A with a line voltage 1100V, 50Hz. Find the circuit constants of the load per phase.

- 15.** (a) Derive the emf equation of transformer.
- (b) A 250V/3000V, 50Hz singlephase transformer has a maximum flux density of  $1.2 \text{ Wb/m}^2$ . If the emf induced per turn is 4 V, find the primary and secondary number of turns and the cross-sectional area of the core.
- 16.** A 100kVA, 1000V/100V, 50Hz single-phase transformer gave the following test results :
- OC test : 1000V, 5A, 1000W on HV side.
- SC Test : Primary voltage for full load current = 22 V, 1050W on HV side.
- Draw the equivalent circuit of a transformer referred to primary.
- 17.** Explain briefly the following parts of power transformer (a) Tank and cooling tube (b) Conservator tank (c) Transformer oil (e) Buchholz's relay with a neat diagram.
- 18.** Explain the load tap changer of a power transformer with neat diagram.

★ ★ ★