



C23-EE-303

23136

BOARD DIPLOMA EXAMINATION, (C-23)

MARCH/APRIL—2026

DEEE – THIRD SEMESTER EXAMINATION

AC CIRCUITS AND TRANSFORMERS

Time : 3 Hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions :** (1) Answer **all** questions.
(2) Each question carries **three** marks.
(3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. Define (a) time period (b) RMS value.
2. Define (a) phase difference (b) cycle.
3. Perform the following operation and put the result in a polar form (i) $A - B$ when $A = (4 - j6)$, $B = (6 + j8)$.
4. Define resonance in an A.C circuit.
5. An A.C circuit consists of a pure resistance of 50Ω and is connected across an A.C supply of 230 V, 50 Hz. Calculate (a) power (b) equation for voltage and current.
6. List the advantages of poly phase over single-phase system.

7. Define polyphase and draw 3 ϕ waveforms.
8. Define all day efficiency of a transformer.
9. List the applications of a transformer.
10. Write the conditions for parallel operations of a 3 ϕ transformer.

PART—B

10 \times 5=50

Instructions : (1) Answer *any five* questions.

(2) Each question carries **ten** marks.

(3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

11. A coil with resistance 50 Ω and inductance 0.1 H is connected in series with a capacitor of 150 μ F across a 200 V, 50 Hz supply. Calculate (i) current, (ii) power factor; (iii) power, (iv) voltage across the coil and capacitor.
12. Explain the method of solving two branch parallel AC circuits by using J-notation method.
13. Derive the relation between line and phase value of current and voltage in 3 ϕ balanced star connected system.
14. A 3 ϕ 400 V, 50 Hz, 100 HP delta connected induction motor is working at full load. Two watt meters are used for measurement of power. Calculate the watt-meter readings if the efficiency of motor is 82% and power factor is 0.8 lag.

- 15.** Derive the condition for maximum efficiency in a transformer.
- 16.** Derive the e.m.f equation of a transformer.
- 17.** Briefly explain off-load tap changing and on-load tap changing of transformer.
- 18.** Explain any two methods of cooling a power transformer with a neat sketch.

★ ★ ★

158