

ELEC3500: Digital Electronics

LAB 3: CMOS Combinational Logic

Lab Section: A3 Tuesday 11:30a.m. – 2:30p.m.

Date Performed: October 1st, 2019

Date Submitted: October 2nd, 2019

Bomi Garuba - 101082652

Kimberley Nguyen- 101031915

1. The MUX

Q1.

 


Fig 1. Output waveforms for CTRL and Y signals

When the CLK is high, the “d” transmission gate turns ON (why? Because its PMOS component is being fed $\text{CLK}_{\text{inverse}}$ Which is low it turns ON and its NMOS component is getting CLK that which is high). Input thus latches to “d”.

When the CLK is low, the “q” transmission gate turns ON (why? Because its PMOS component is being fed CLK Which is low it turns ON and its NMOS component is getting $\text{CLK}_{\text{inverse}}$ that which is high). Input thus latches to “q”.

Q2.

 


Fig 2. Measuring time from Control High to Y Valid

 


Fig 3. Measuring time from Control Low to Y Valid

By simulation and observation, the times from control low/high to Y valid were measured to be:

- $t_{CHYV} = 232.677 \text{ ps}$
- $t_{CLYV} = 137.792 \text{ ps}$

2. The D-Latch

Q3.

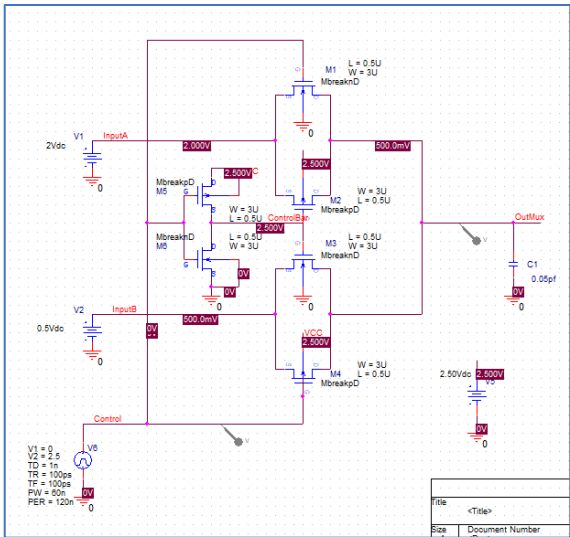


Fig 4. MUX Circuit schematic

 


Fig 5. D-Latch using MUX

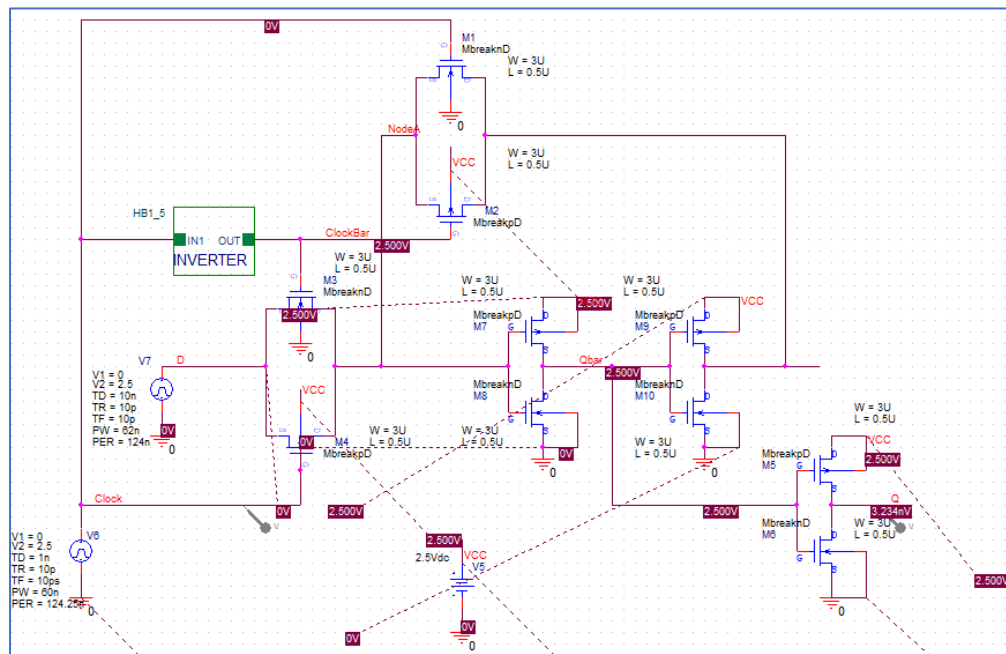


Fig 6. D-Latch Circuit schematic with added parts

A 2:1 multiplexer selects between two inputs depending upon the value of its select input. Also, a latch holds its previous value when its enable pin is in a particular state ('0' for positive level sensitive latch and '1' for negative level sensitive latch). To achieve this, a connection was made from the output of the MUX (Qbar) to the 0 input, to create a feedback. Inverters were also added to Qbar to generate Q output. See figure below.

 


Fig 7. D-Latch created from MUX

Q4.



Fig 8. Waveform showing transparent latching

Q5.



Fig 4. Measuring setup time for Latch circuit

Setup time is seen to be 9.347ns.



Q6.

 


Fig 5. Measuring setup time for Latch circuit containing 0.5pF

Capacitor



The delay setup time was noticed to have increased by 10 ns on Fig 5.It is now 19.33ns

Q7.


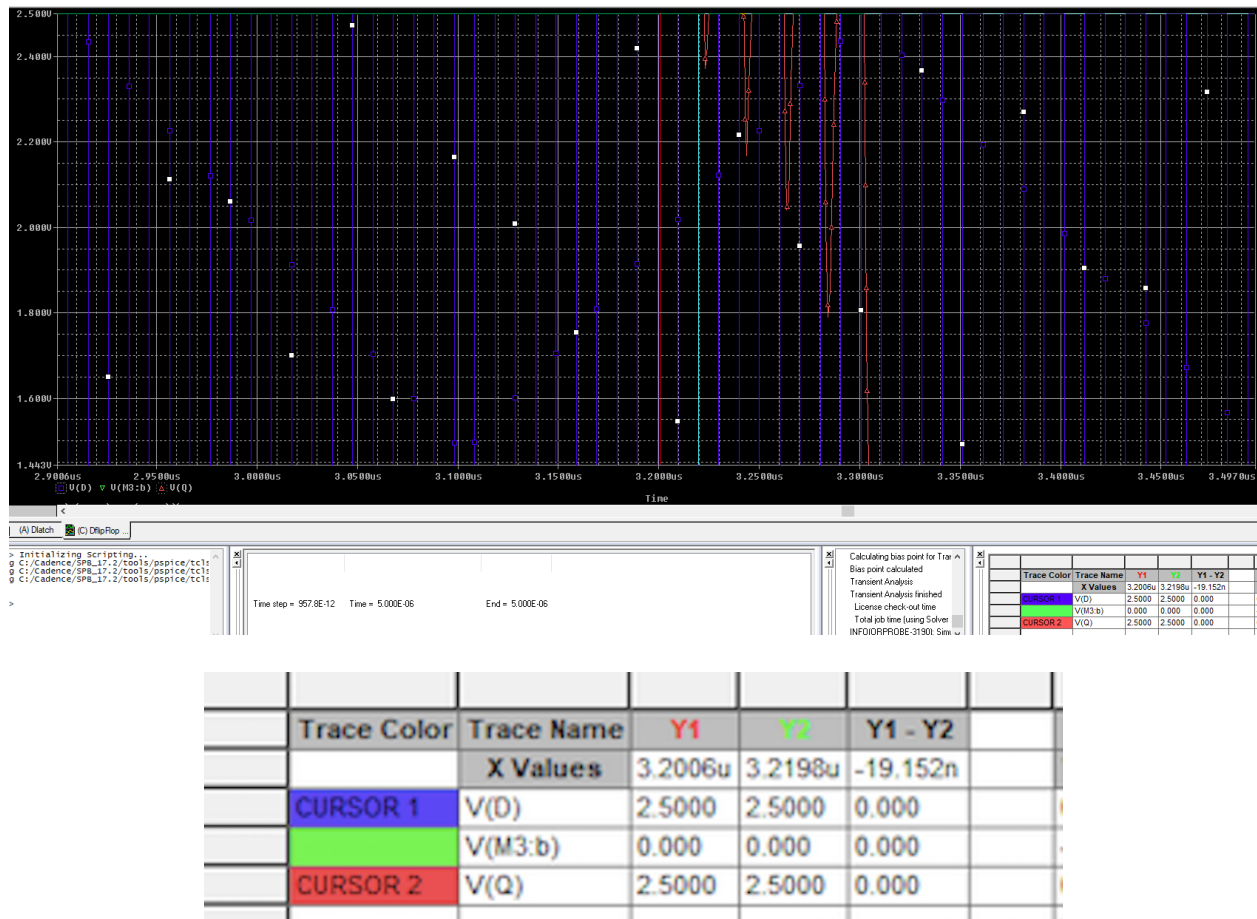


Fig 6. Measuring setup time for D flip-flop at the first invalid V_{out} point

The setup time as shown is 19.152 s.

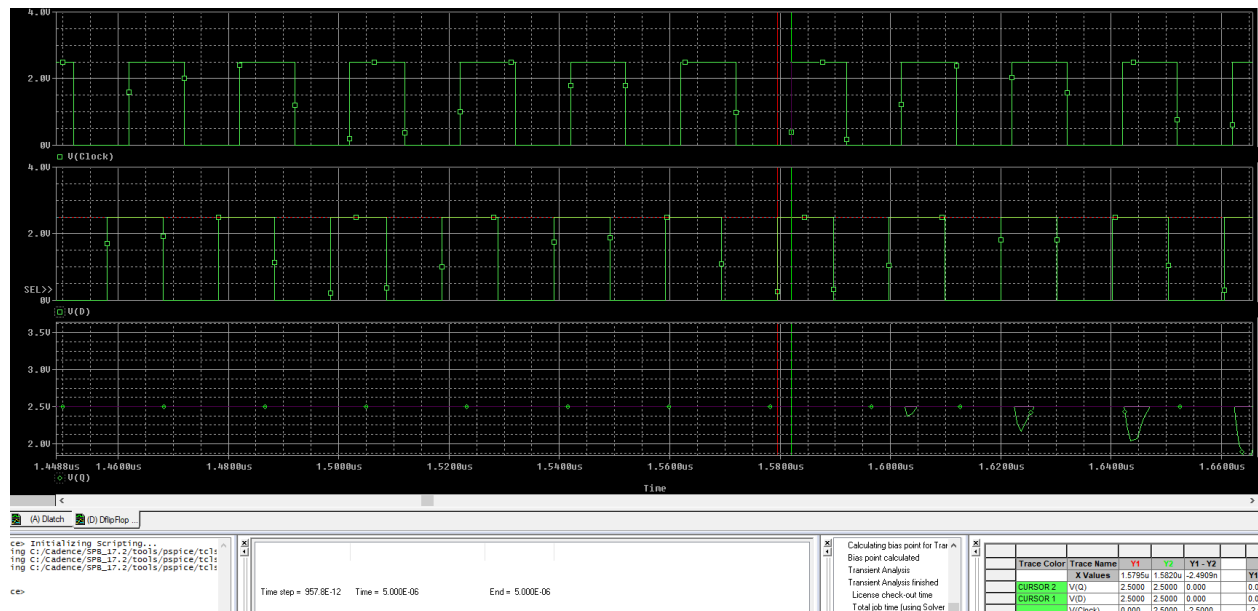



Trace Color	Trace Name	Y1	Y2	Y1 - Y2
	X Values	1.5795u	1.5820u	-2.4909n
CURSOR 2	V(Q)	2.5000	2.5000	0.000
CURSOR 1	V(D)	2.5000	2.5000	0.000
	V(Clock)	0.000	2.5000	-2.5000

Fig 7. Measuring setup time for D flip-flop at the last valid V_{out} point

The overall setup time I gotten by subtracting the setup time in Fig 7. From the time in Fig.6:

$$19.152\text{ns} - 2.4909\text{ns} = 16.66\text{ns}.$$