

4.2.2 Electrical Current

The charge passing a point per unit time

$$I = \frac{Q}{t}$$

(A) → (C) → (s)


$$A = \frac{C}{s}$$

$$Q = 20C$$

$$t = 2 \text{ min}$$

$$I = \frac{20}{120} = 0.17s$$

$$I = \frac{Q}{t}$$

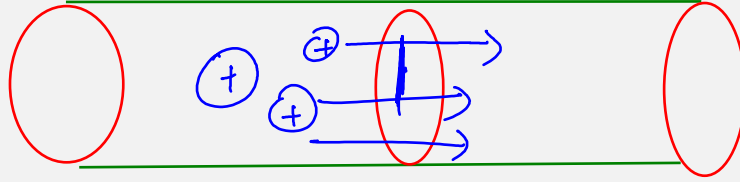

Total charge
time

$$2.5A = I$$

$$t = 5s \quad Q = ?$$

Unit of Current

$$2.5 = \frac{Q}{5}$$

Ampere (A)

$$7.5C = Q$$

$$A = C/s$$



$$\text{unit of current} = \frac{\text{unit of charge}}{\text{unit of time}}$$

$$A = \frac{C}{s}$$

$$5A \rightarrow \frac{5C}{1s}$$



If one coulomb charge passes through a point in one second then current will be 1 Ampere

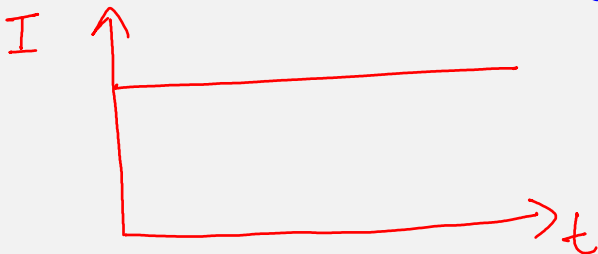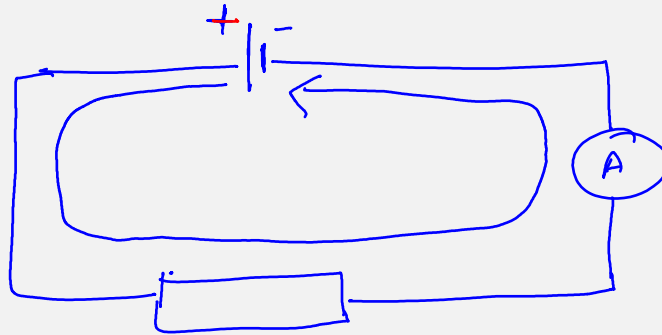→ Direct Current: Current that flows only on one direction is called as d.c.




↑ always above x-axis

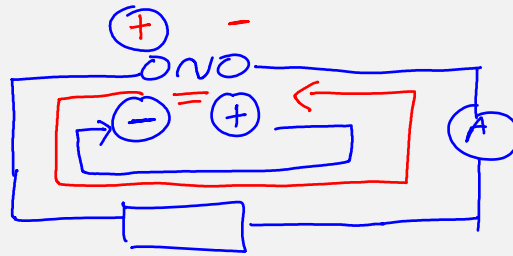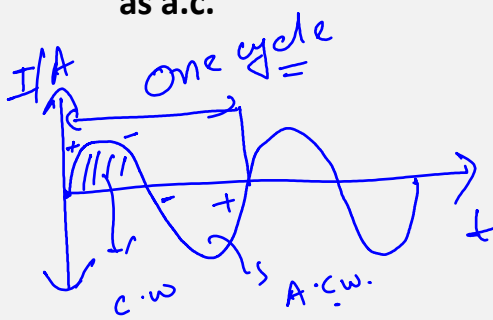Alternating Current: Current that reverses its direction of flow regularly is called as a.c.




frequency \rightarrow Hz
50 Hz
1s \rightarrow 50 cycles

Ammeters (Analogue and Digital)

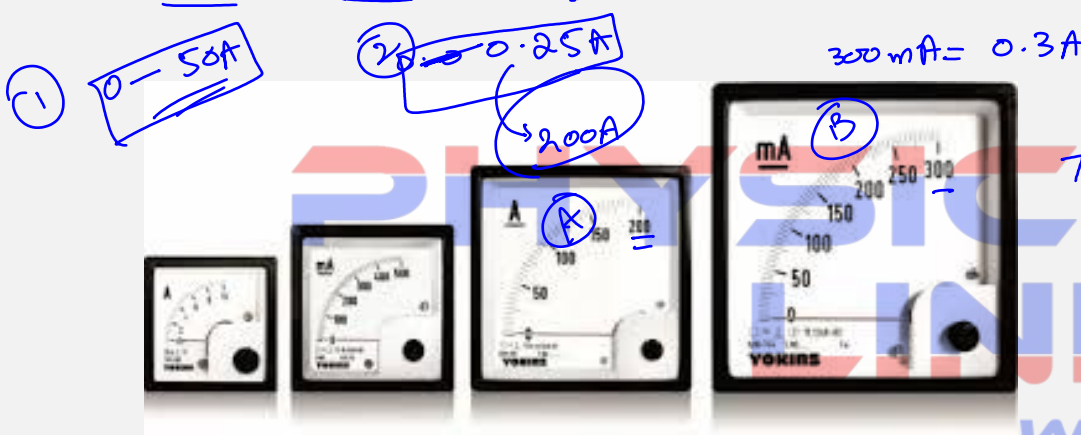


Try to use the ammeter with smallest possible range.

HASEEB HANIDER

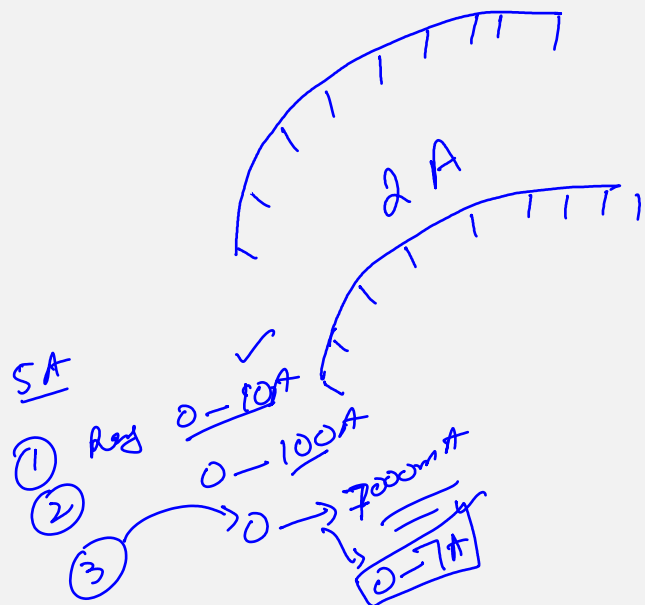


Conventional Current vs Flow of Electrons

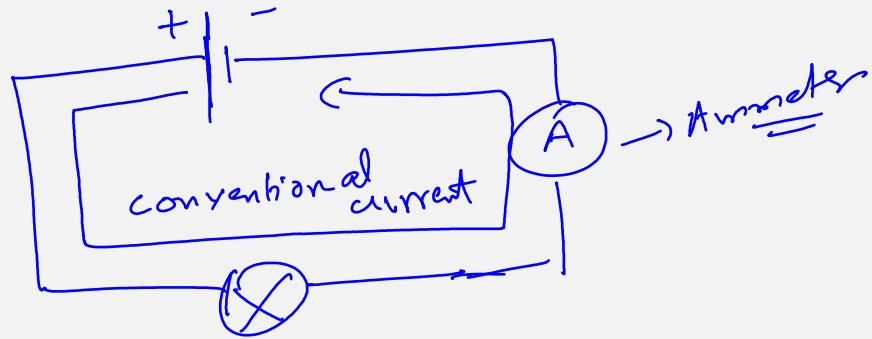Conventional Current is the flow of positive charges from the positive terminal of the source towards the negative terminal.




Electronic current

↳ flow of electrons

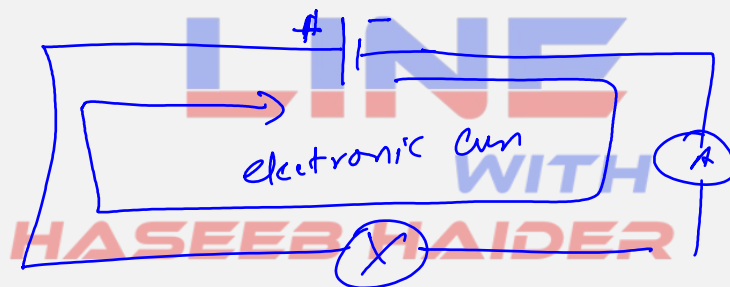

effect of $n e^-$ passing through a point 10 mA
 is the same
 as of n protons flowing through the
 same point in same
 amount of time.

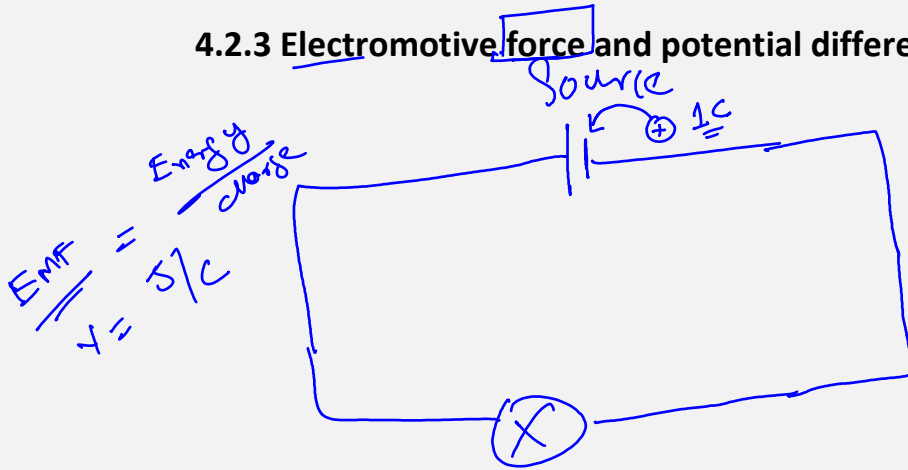4.2.3 Electromotive force and potential difference



EMF is the electrical work done by a source in moving a unit charge around a complete circuit.

Source → charge

EMF

unit ⇒ Volts (V)

$E = \frac{W}{Q}$

Energy transferred

charge

$V = \frac{1J}{1C}$

EMF = 20V

Q = 2C


Energy = ?

$E = \frac{W}{Q}$

$20 = \frac{W}{2}$

$W = 40J$

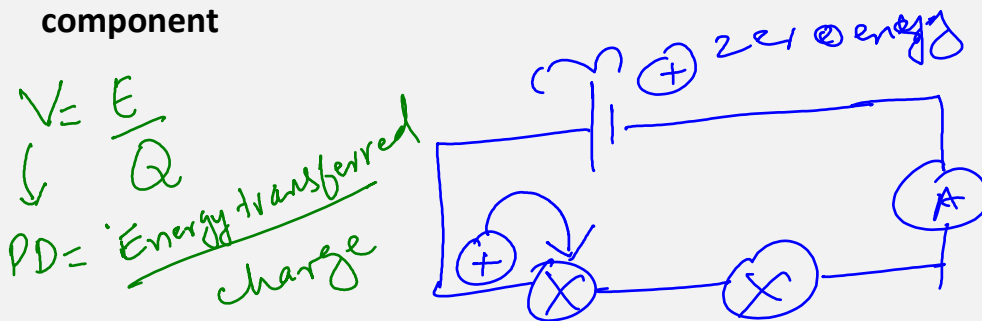Potential Difference is the work done by a unit charge passing through a component



Unit of EMF and PD

$$Volt = \frac{J}{C}$$


EMF
w.d on
the
charge

vs

PD
w.d by
the
charge

Voltmeters

11

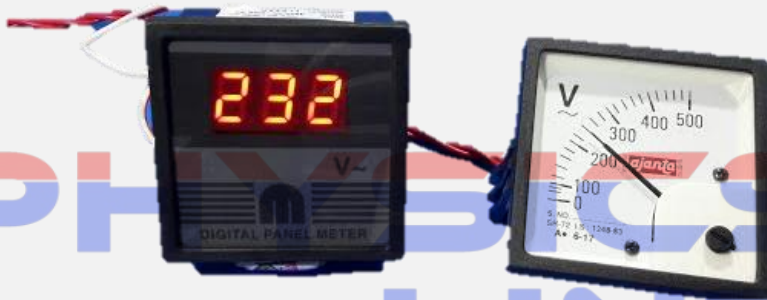

Range


important

1C \rightarrow 12J
1C \rightarrow 220J

Font
#2

12V
220V

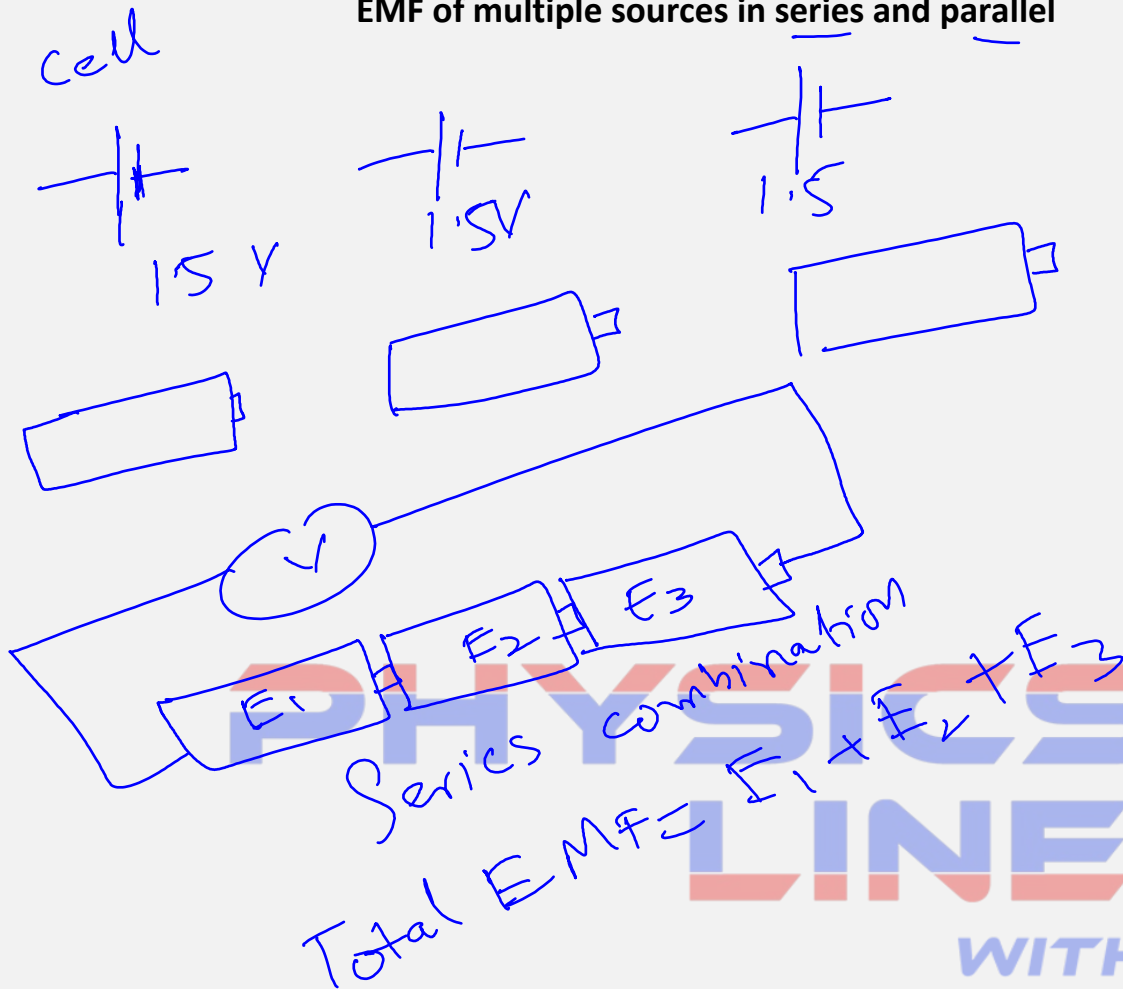EMF of multiple sources in series and parallel





Parallel combination

Total EMF = EMF of
one
cell

Benefit of connecting cells
in parallel??

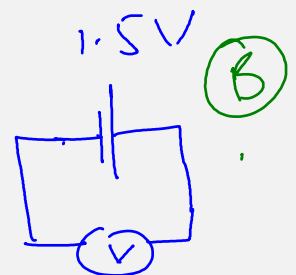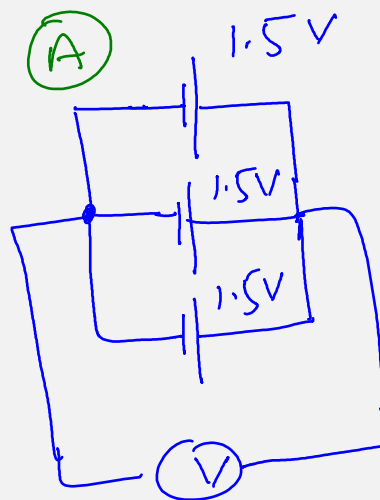
Takes longer to exhaust
or provides maximum
potential for longer period of
time than a single cell of
same emf



EMF in both A and B will
be 1.5 V.


But Circuit A will last
longer as only **one of three**
cell will be used during
one cycle.

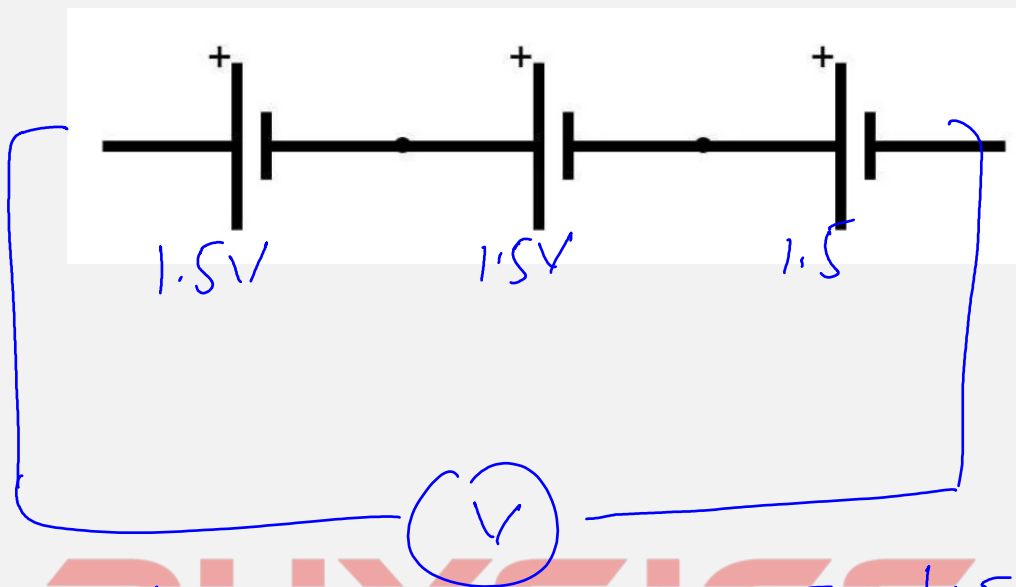When cells are connected in series we add the individual EMFs to get the total EMF




$$\text{Total EMF} = 1.5 + 1.5 + 1.5 = 4.5\text{V}$$

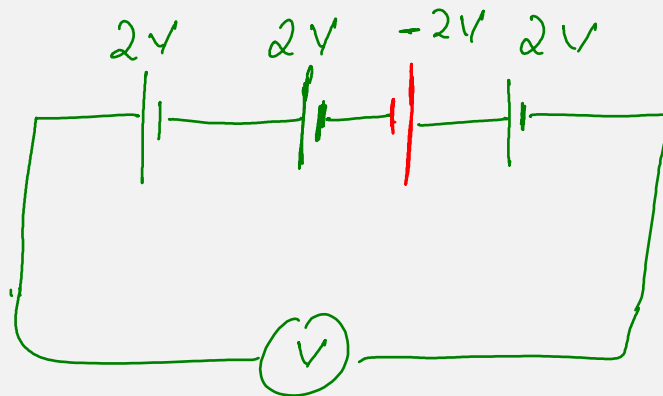If one of the cells is connected the other way around then that cell causes a decrease in overall EMF


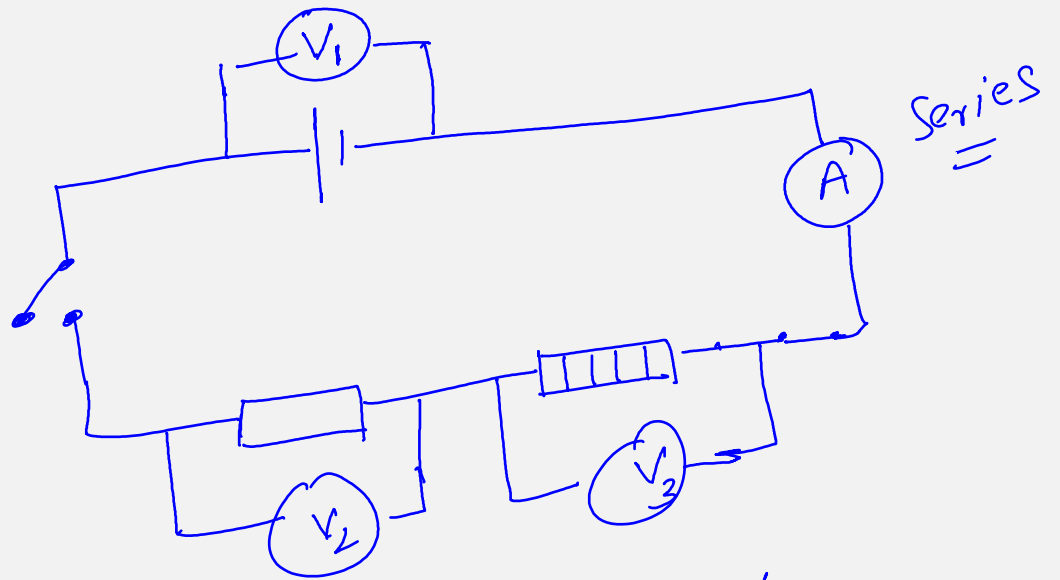
$$\begin{aligned} \text{Total EMF} &= 2 + 2 - 2 + 2 \\ &= 4\text{V} \end{aligned}$$



$V_1 \Rightarrow$ EMF
 $V_2 \Delta V_3 \Rightarrow$ P.D across the two components
Series

PHYSICS
LINE
WITH
HASEEB HAIDER