
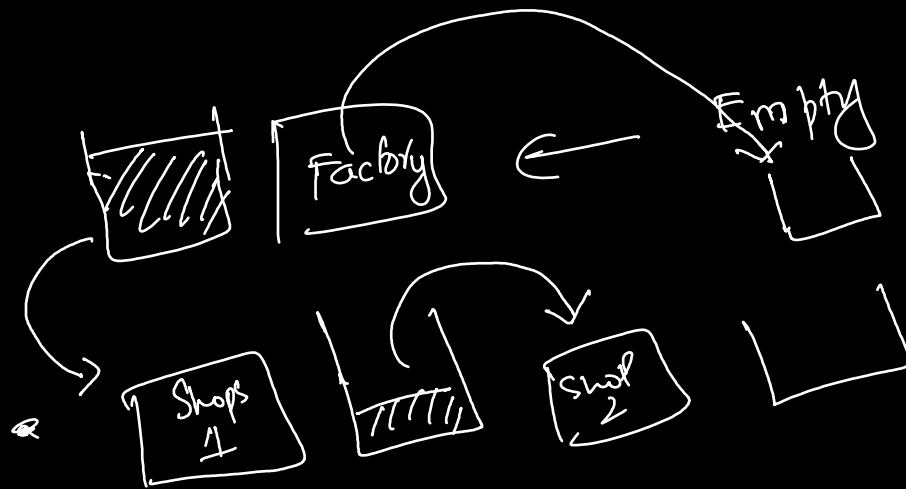


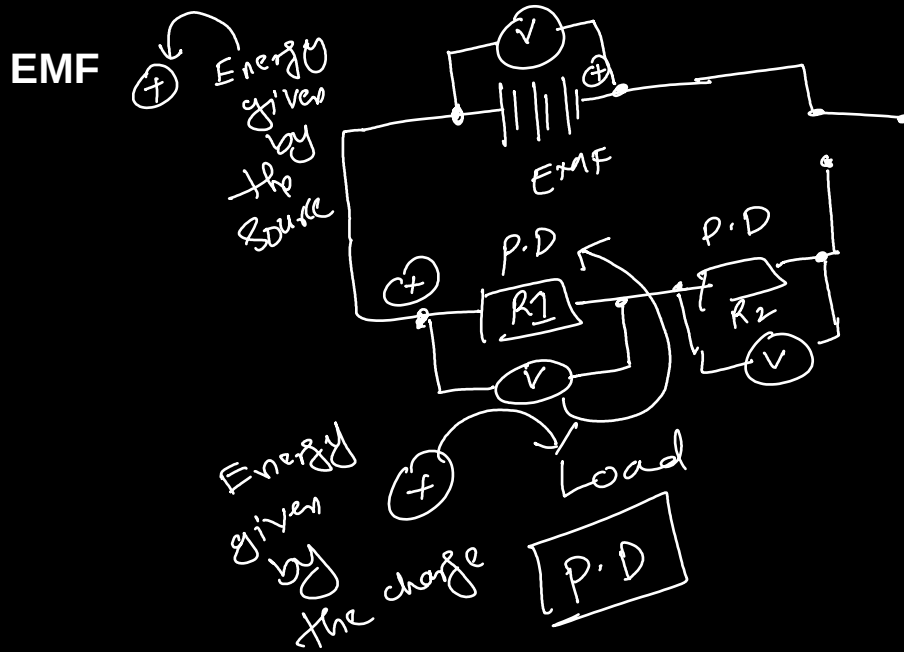5054 – O Level Physics  
Recap of previous lesson



#### 4.2.4 Resistance



consumer of Energy of charge

Hindrance in the flow of charge.

Resistance is the ratio of potential difference and current.

$$\text{Resistance} = \frac{\text{p.d.}}{\text{current}}$$

$$R = \frac{V}{I}$$

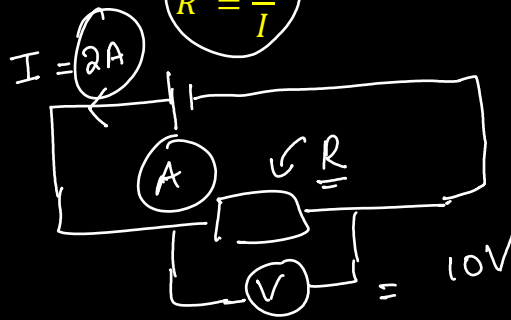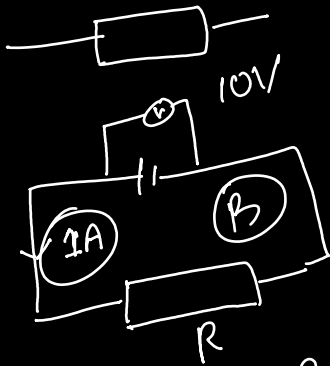

$$\frac{V}{I} = R = \frac{10}{2} = R$$

$$5\Omega = R$$

Unit of Resistance

$$R = \frac{V}{I} = \frac{10}{2} = 5\Omega$$

ohm  $\Omega$

Define

ohm

$$\text{ohm} = \frac{\text{Volts}}{\text{Ampere}}$$

If one volt of p.d. produces a current of 1 ampere then resistance is 1 ohm.

$$\uparrow R \propto \frac{1}{I} \downarrow$$

$$V = IR$$


### Experiment to determine resistance

↳ Instruments  
↳ their usage

$$R = \frac{V}{I}$$


$\xrightarrow{\text{Voltmeter}}$   
 $\xrightarrow{\text{Ammeter}}$

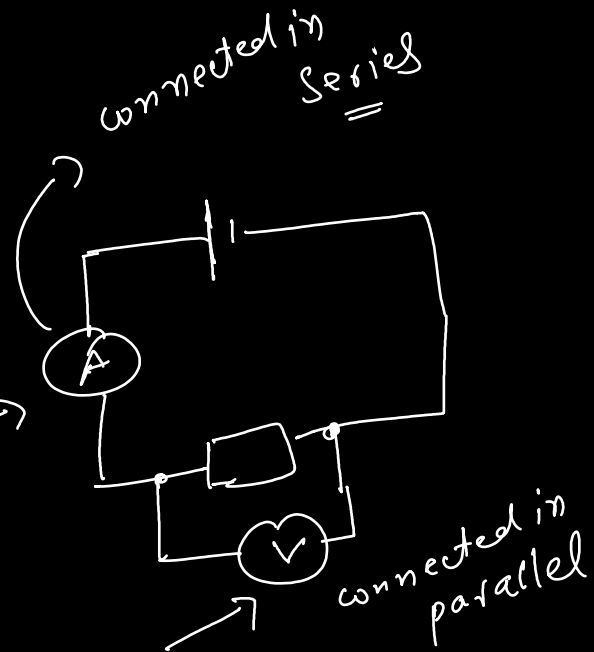Ratio of readings  
from the voltmeter  
and the  
Ammeter



### Factors affecting Resistance of a wire of a filament


i. length

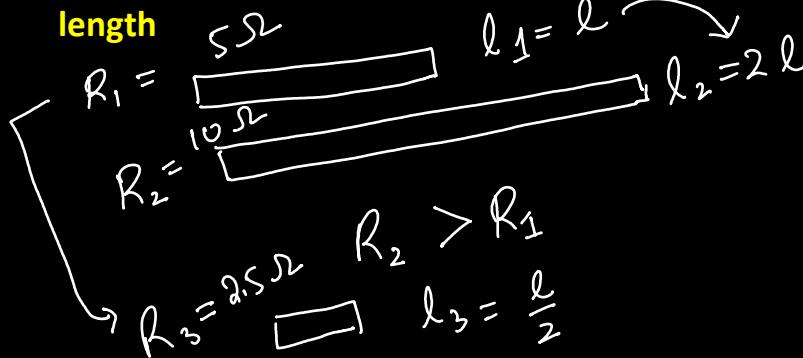

$$R \propto l$$

ii. cross-sectional area


$$R_1 = 30\Omega \quad A_1 = A$$

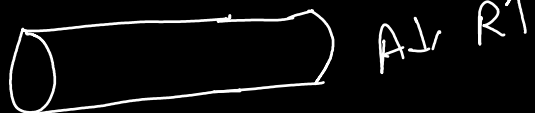

$A \downarrow \quad R \uparrow$

$$R_2 = \frac{30}{3} \quad A_2 = 3A$$

$$R_2 = 10\Omega$$

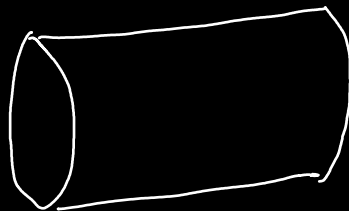

$A \uparrow \quad R \downarrow$

$$R \propto \frac{1}{A}$$

Wire X has resistance  $R$ .

Wire Y is made from the same material and has same cross-sectional Area.

Wire Y has double the length of the wire X.

What will be its resistance in terms of  $R$ .

$$\underline{2R}$$

double the  $l$   
" "  $R$

Wire X has resistance  $R$ .

Wire Y is made from the same material and same length.

Wire Y has three times the cross-sectional Area of the wire X.

What will be the resistance of wire Y in terms of  $R$ .

$$\underline{\frac{R}{3}}$$


A inc by 3 times  
R dec " 3 times  
↳  $\div$

Wire X has resistance  $R$ .

Wire Y is made from the same material.

Wire Y has three times the cross-sectional Area of the wire X and half the length of Wire X

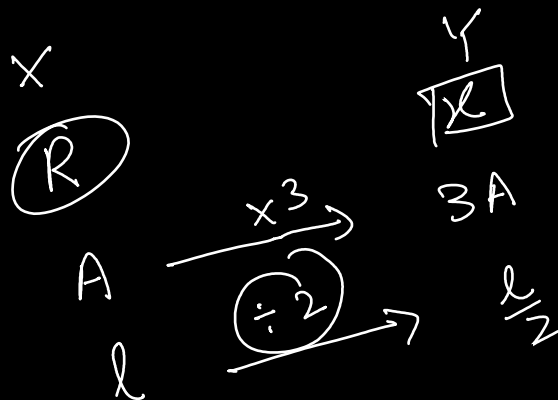What will be the resistance of wire Y in terms of  $R$ .



$$\frac{R}{3} \div 2$$

$$\frac{R}{3} \times \frac{1}{2}$$



$$\boxed{\frac{R}{6}}$$

## Ohms Law

For fixed resistor at constant temperature, the current flowing through is directly proportional to the voltage applied across it.



$$V \propto I$$

$$V = IR$$

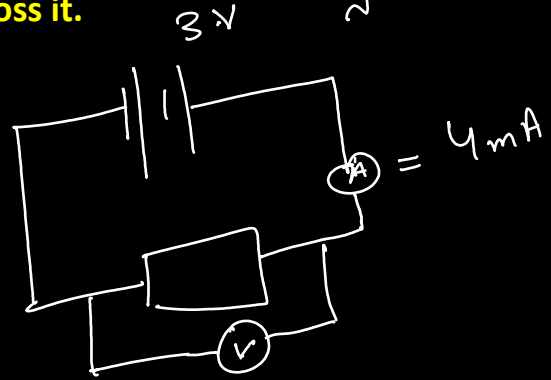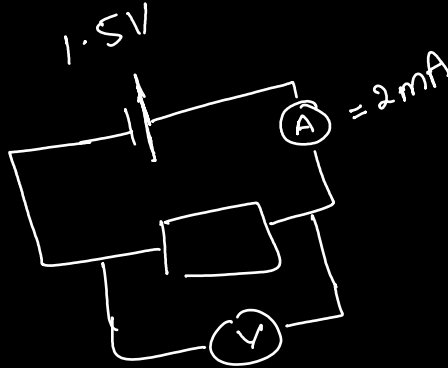

## Combination of resistors


Series

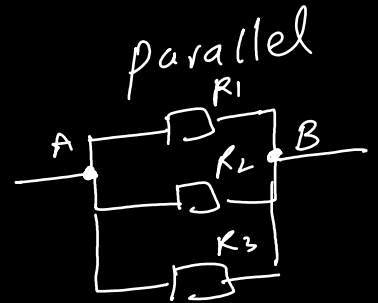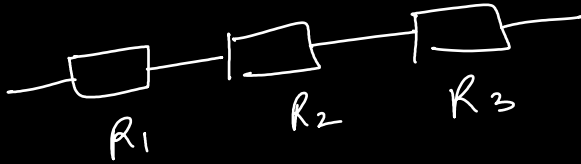

Equivalent Resistance  
 A single resistor that gives the same effect as of the individual resistances joined together.

Series circuit

$$R_e = R_1 + R_2 + R_3$$

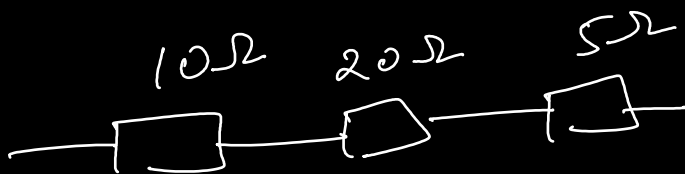

$$R_e = 10 + 20 + 5 = 35\Omega$$

Parallel circuit



$$\frac{1}{R_e} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_e} = \frac{1}{5} + \frac{1}{10} = \frac{10+5}{50}$$

$$\frac{1}{R_e} = \frac{3}{10} \quad R_e = \frac{10}{3} \quad \frac{1}{R_e} = \frac{15}{50} = \frac{3}{10}$$

Short cut formula for finding  
equivalent resistance of parallel combination

$$R_e = \frac{\text{Product}}{\text{Sum}}$$

$$R_e = \frac{50}{15} = \frac{10}{3} \Omega$$

l decreases by 3 times  
A inc by 3 times  
 $X \rightarrow R$

$$\frac{R}{3 \times 3} = \frac{R}{9}$$

l increased by 4 times  
A " " 3 times

$Y = ?$

$$\frac{4R}{3}$$