




ELECTRICITY

EQVI. RESISTANCE

PRACTICE SHEET

By Professor Phi

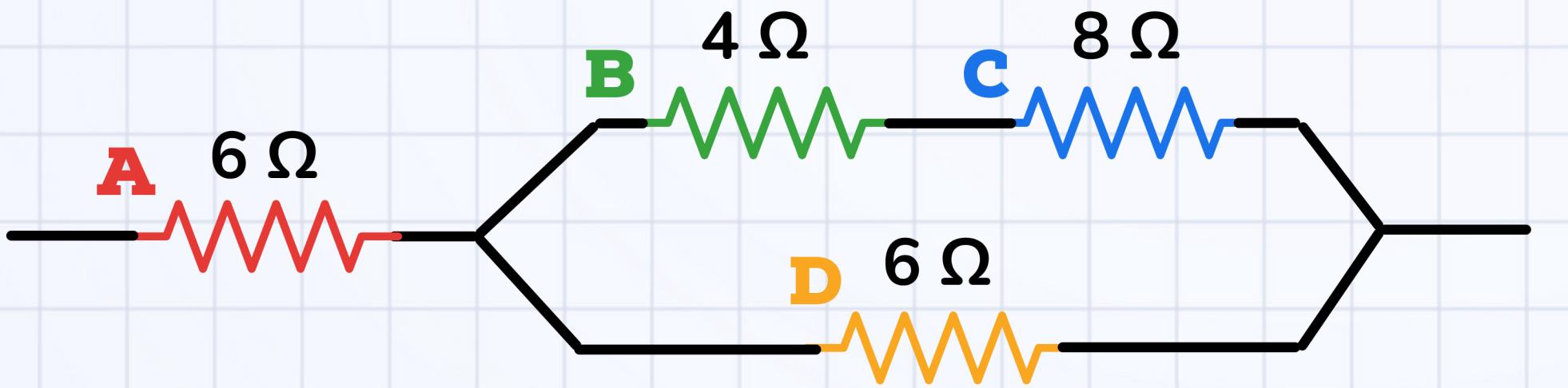

For more please visit professorphi.com
Or search 'Professor Phi' on [YouTube](https://www.youtube.com)




NOTES

Always Solve 'Pure Combination' First



Series Combination

$$R_{eq} = R_A + R_B$$

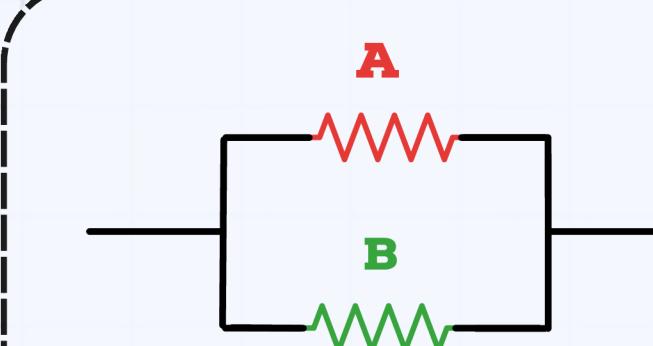

Parallel Combination

$$\frac{1}{R_{eq}} = \frac{1}{R_A} + \frac{1}{R_B}$$

MISTAKES

AVOID THIS

Mistake No : 1

Wrong formula 'Parallel Combination'

Mistake No : 2

Reciprocal Mistake

Mistake No : 3

Direct Solving of Resistance

FIND EQUIVALENT RESISTANCE

Between Points 'X' & 'Y'

Key points for improvements

- Solve slow to gain confidence
- Note down your mistakes
- Do not repeat mistakes
- Increase speed little by little
- Practice everyday



FIND EQUIVALENT RESISTANCE


LEVEL 1




(1.1)




(1.2)

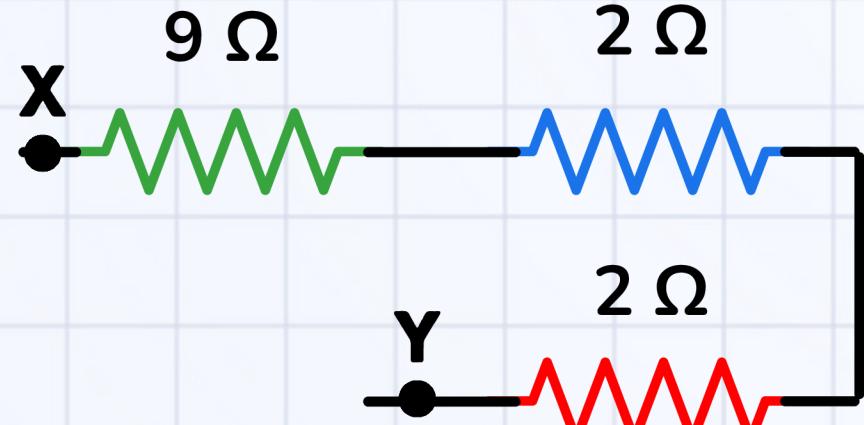

(1.3)

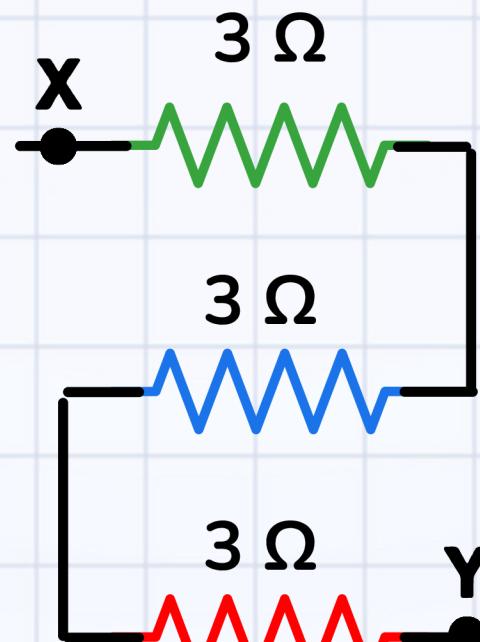


(1.4)

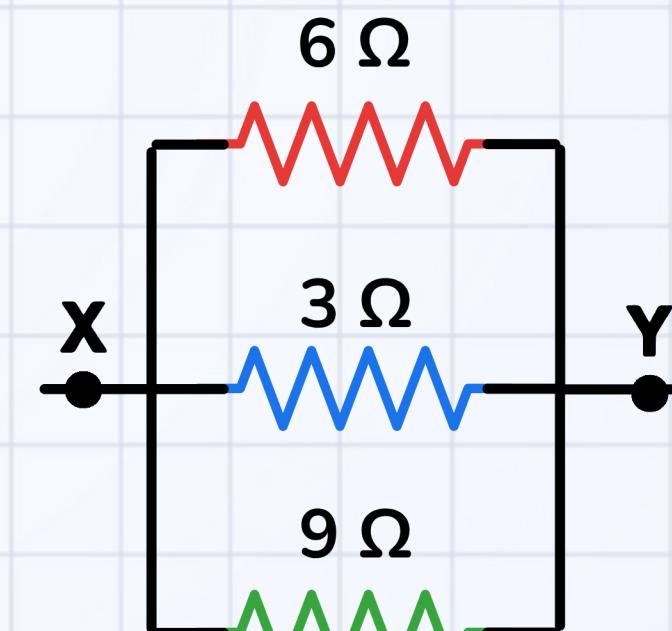


(1.5)

FIND EQUIVALENT RESISTANCE


LEVEL 2

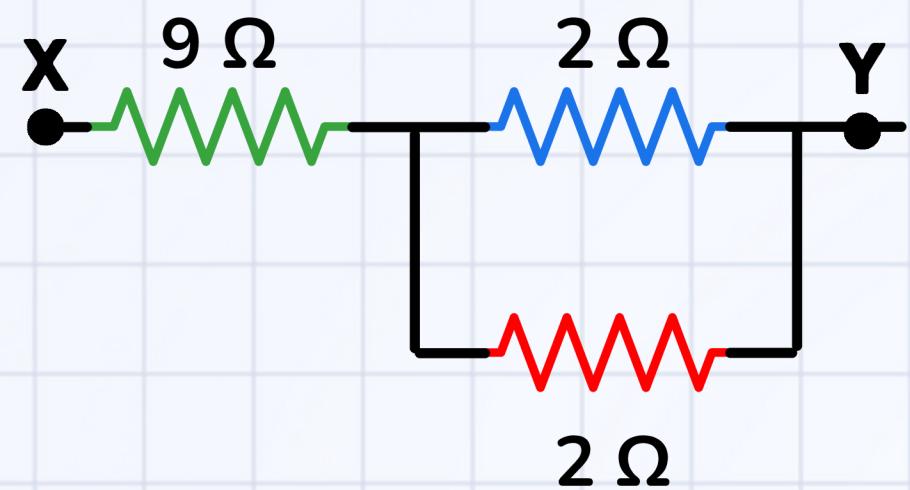


(2.1)

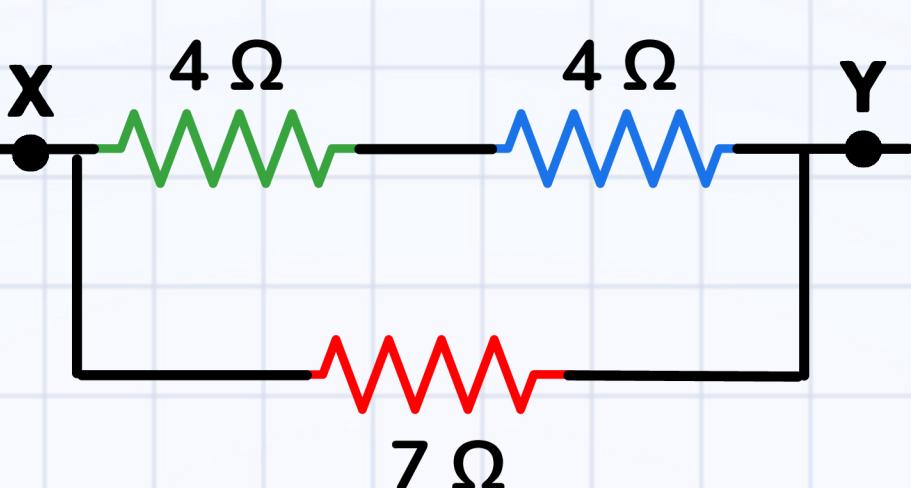


(2.2)

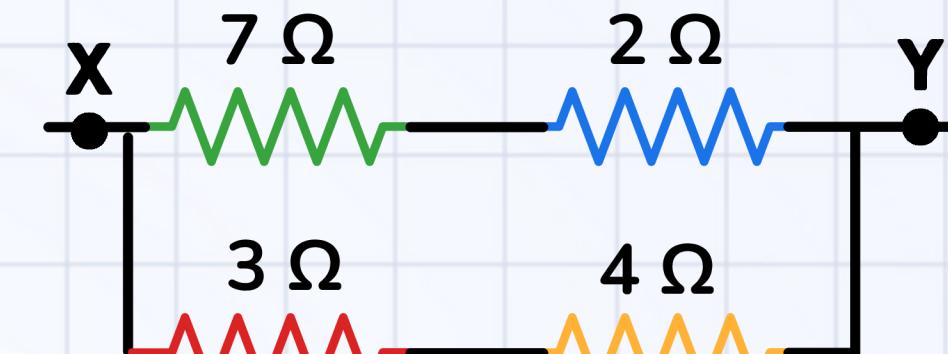

(2.3)

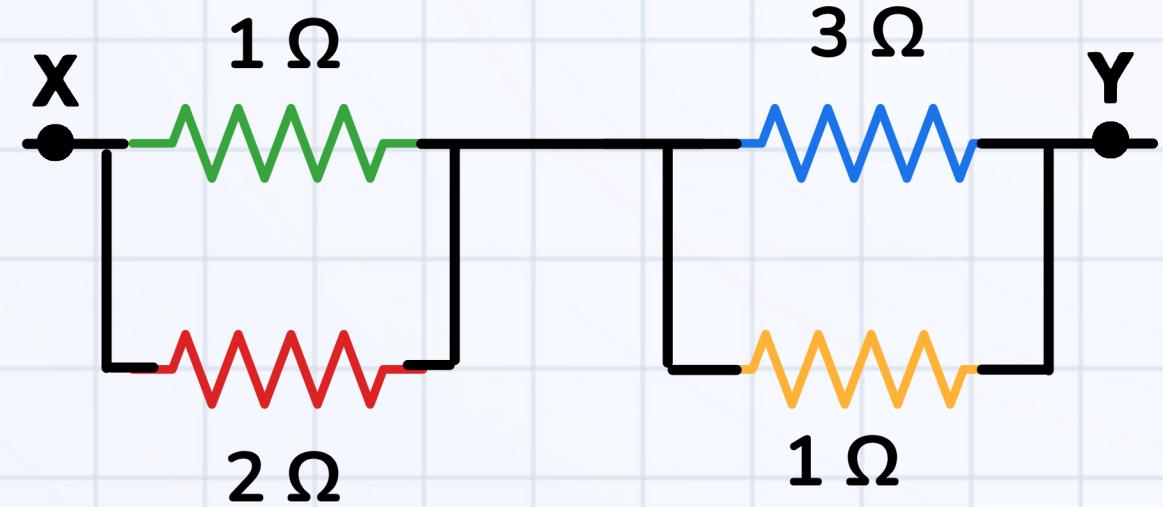

(2.4)

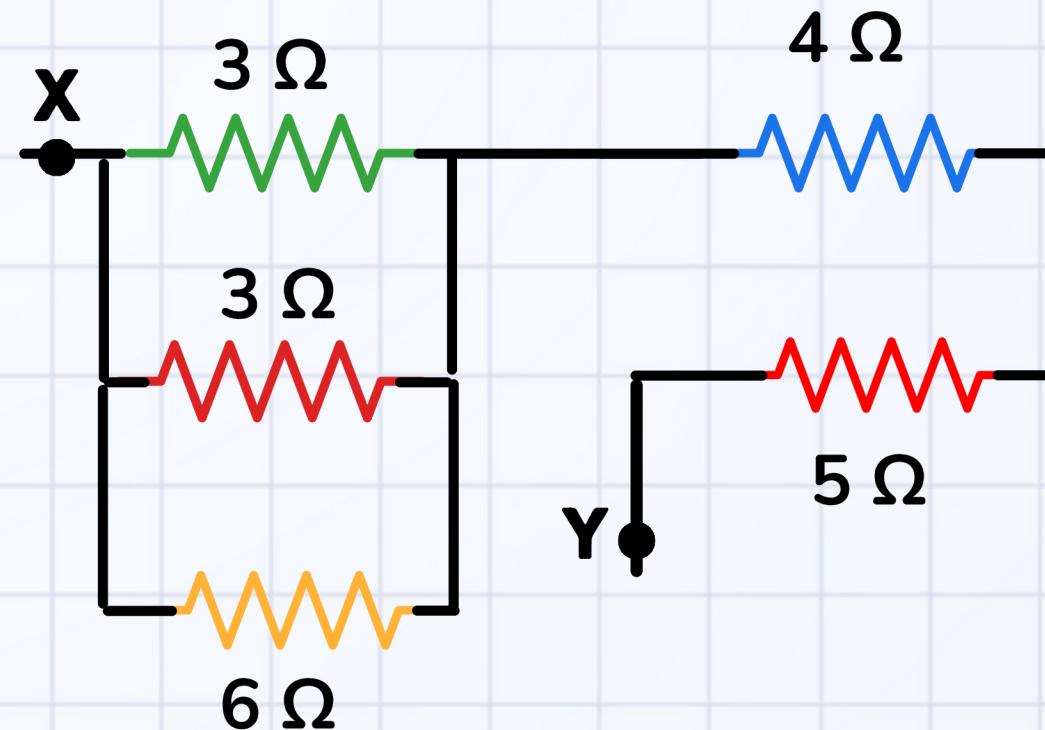


(2.5)


FIND EQUIVALENT RESISTANCE

LEVEL 3

Search me on YouTube : @ProfessorPhi

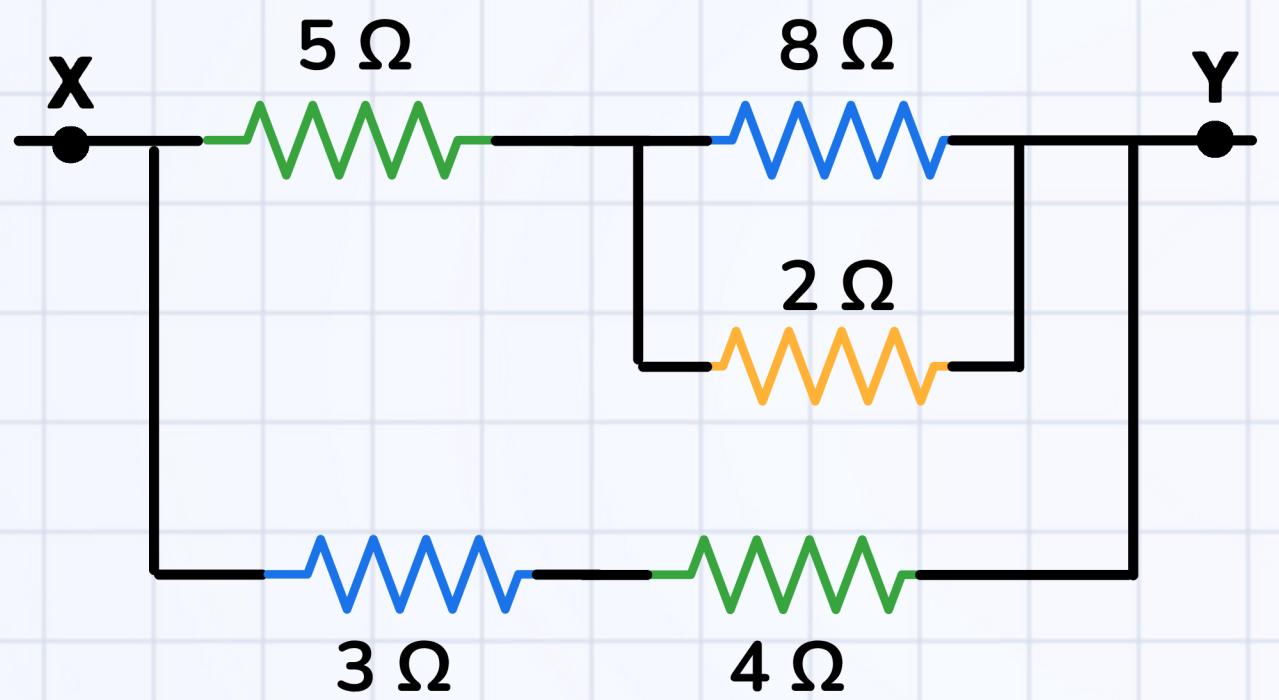

(3.1)

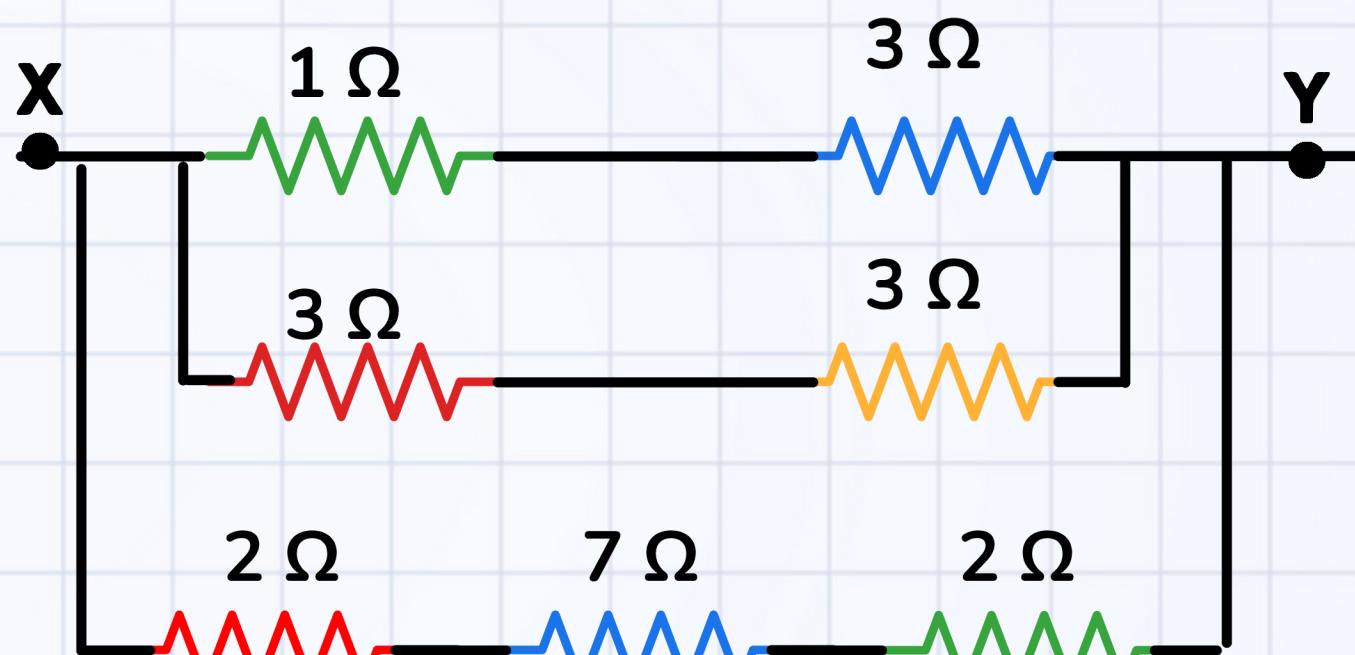


(3.2)


FIND EQUIVALENT RESISTANCE

LEVEL 3

Search me on YouTube : @ProfessorPhi

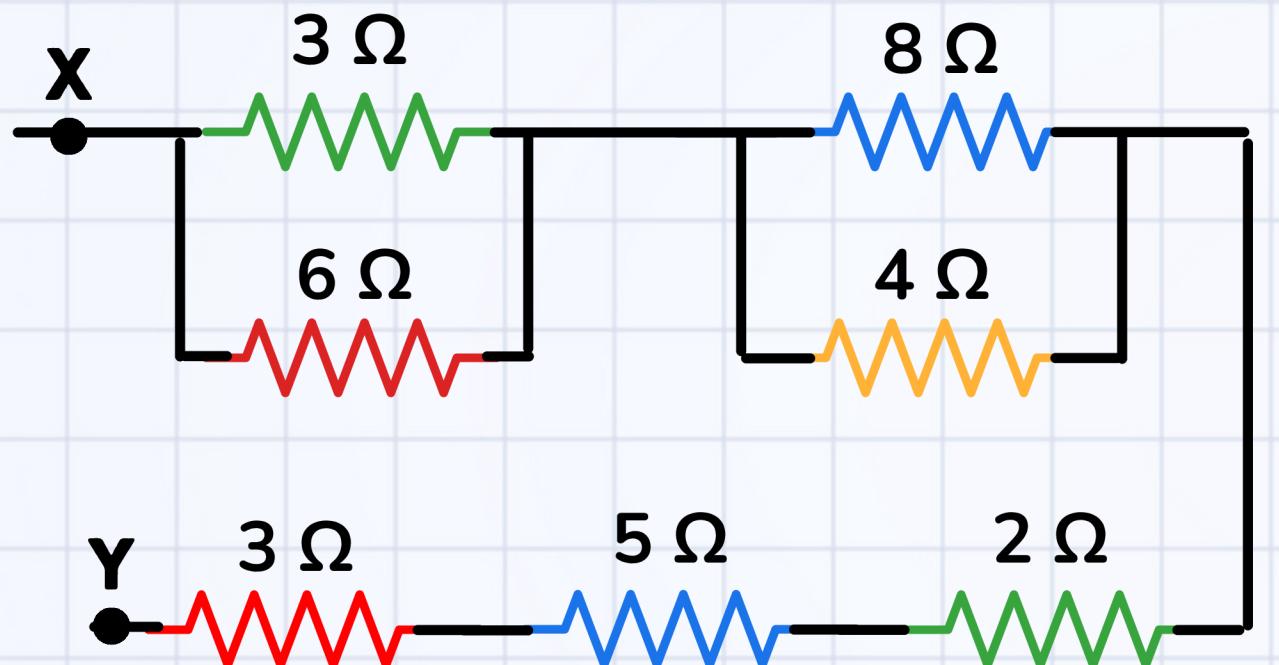

(3.3)

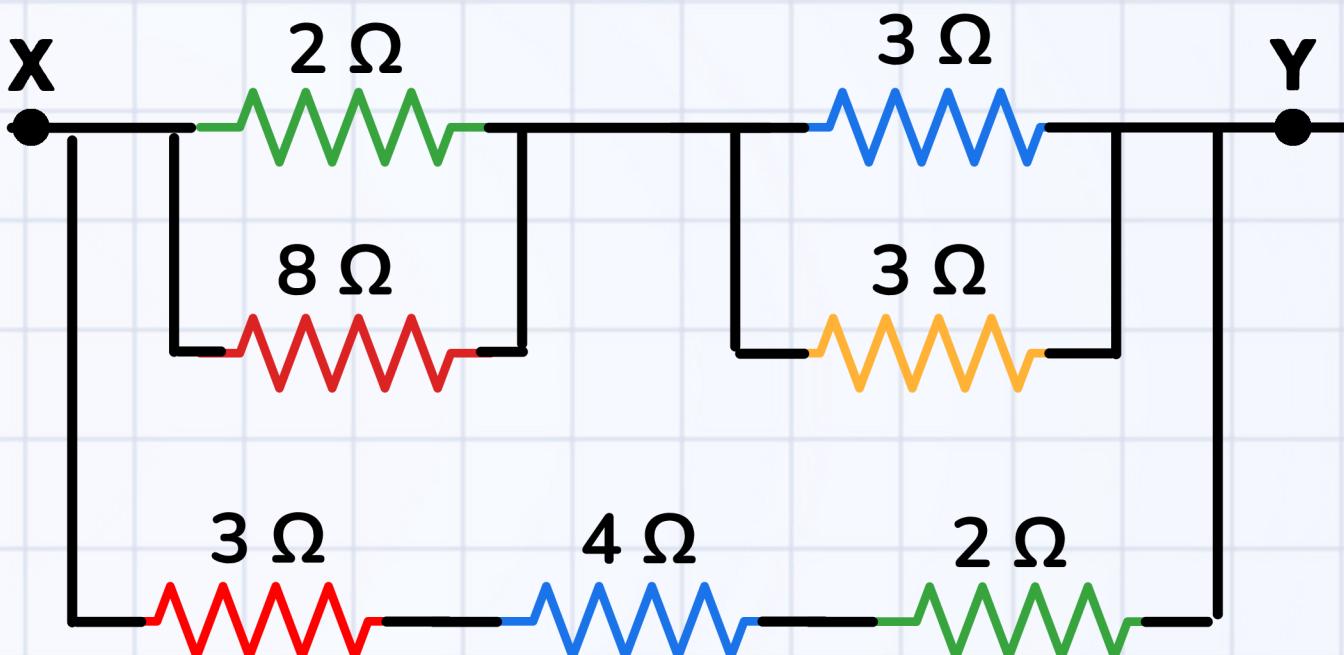


(3.4)

FIND EQUIVALENT RESISTANCE

LEVEL 3


Search me on YouTube : @ProfessorPhi

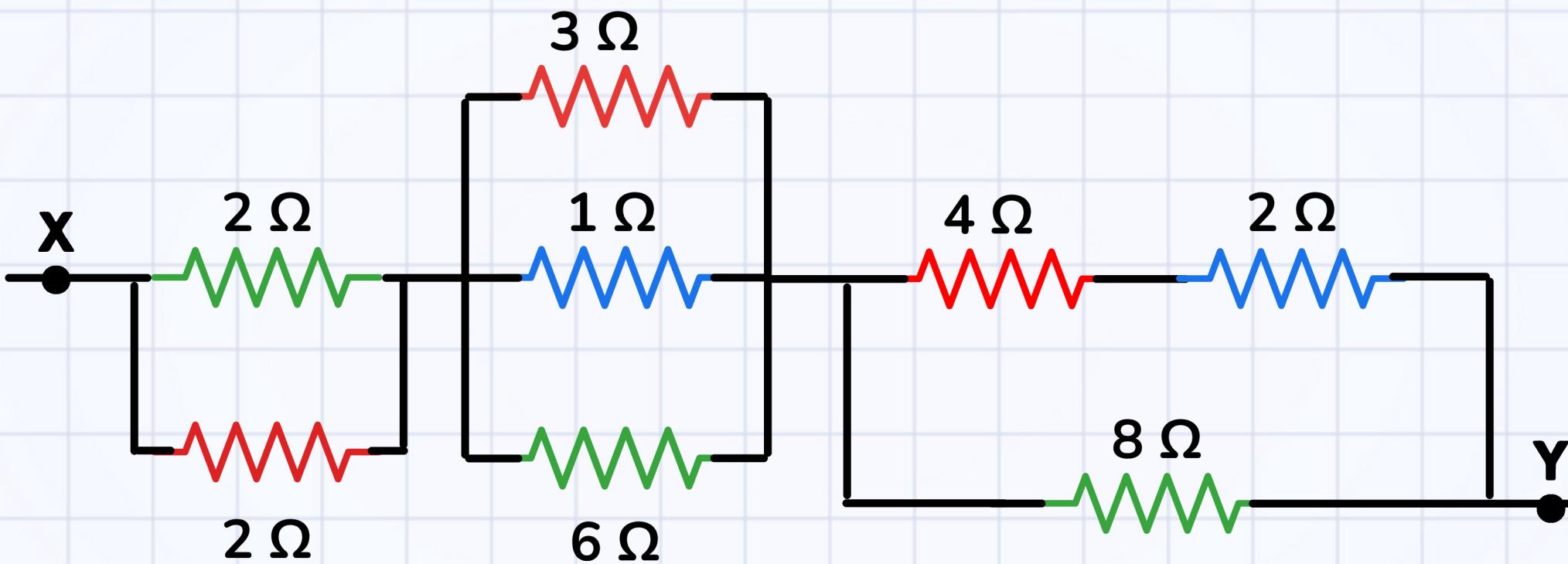

(3.5)

FIND EQUIVALENT RESISTANCE

LEVEL ???

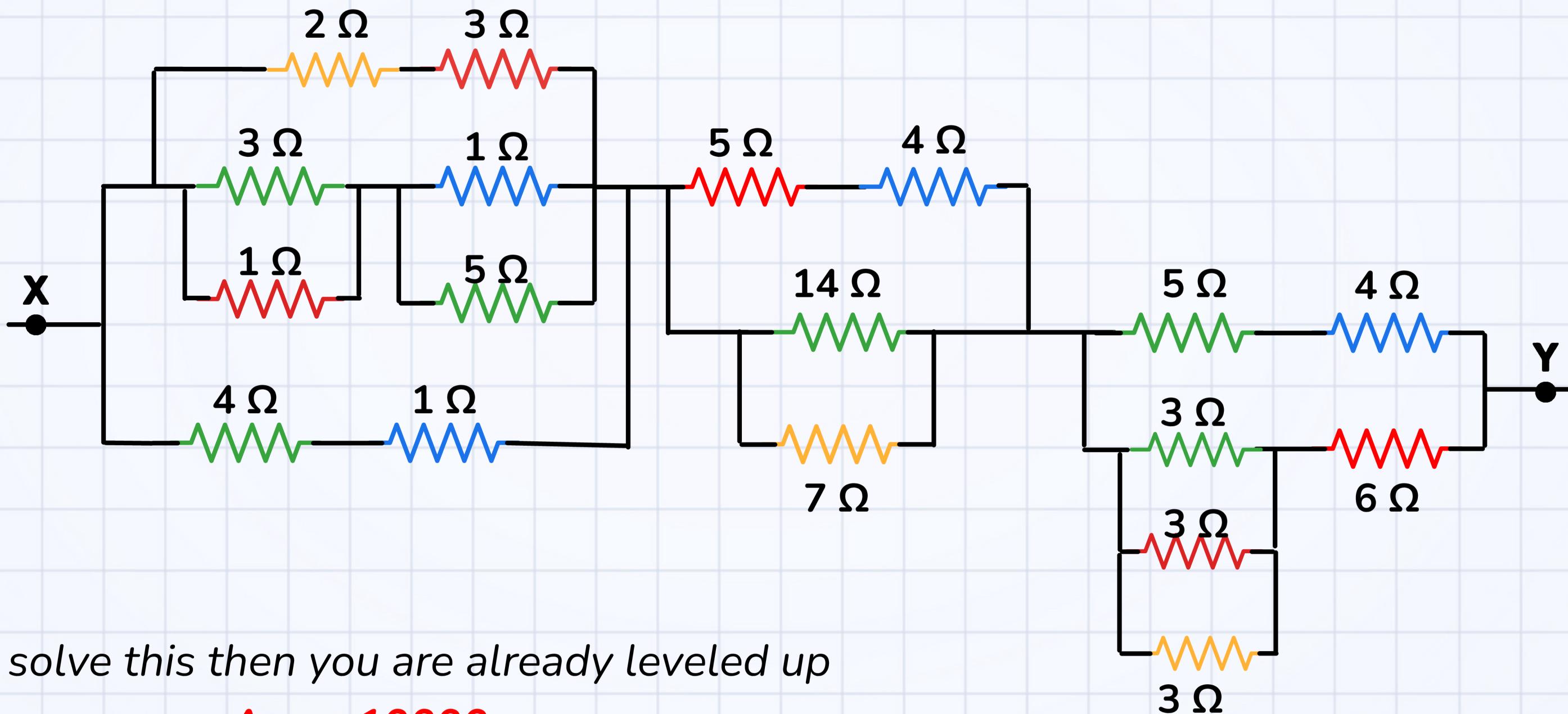

If you solve this then you are already leveled up

Aura+10000

2.1 : 10 Ω

1.3 : 13 Ω

2.5 : 10.2 Ω

2.4 : 1.4 Ω

3.3 : 14.6 Ω

2.2 : 3.7 Ω

1.2 : 14 Ω

3.4 : 2.3 Ω

3.2 : 1.90 Ω

1.4 : 9 Ω

2.3 : 3.9 Ω

1.5 : 1.63 Ω

3.1 : 3.39 Ω

Answers ??

wo toh yaha nai hai



Dear Student,

I hope you find these notes helpful in your studies.

My motto in creating these notes is simple: to make learning more interesting, enjoyable and easy to understand for everyone.

If these notes spark your interest in studies, I would truly appreciate it if you could leave a review on my website—I'd love to hear your thoughts and feedback.

As for your marks, the credit belongs entirely to you—your dedication, hard work, and a little bit of luck.

Wishing you all the best for your future.
Keep shining, keep learning!

With warm regards,
Professor Phi
Indian YouTube Educator

