
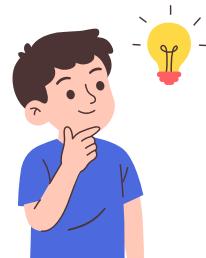
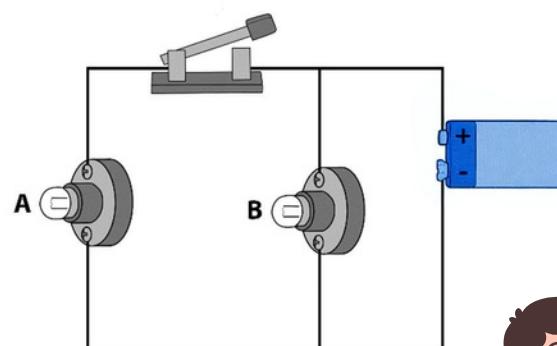
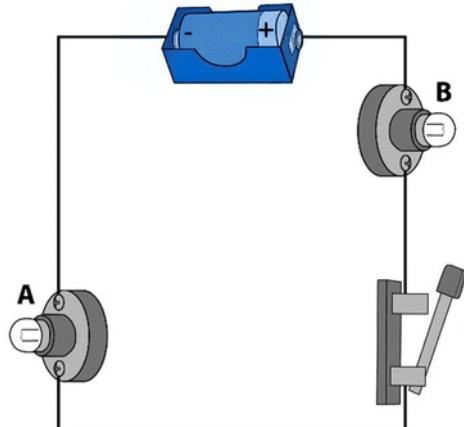
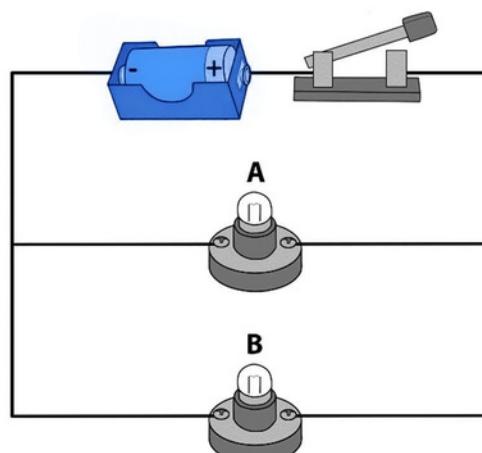
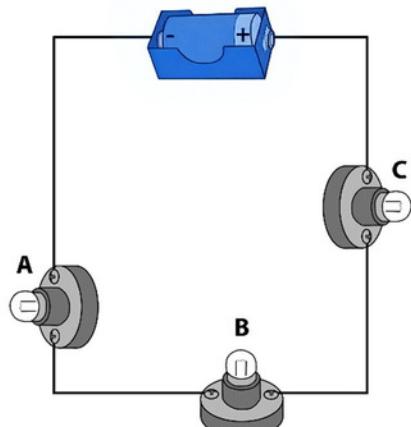
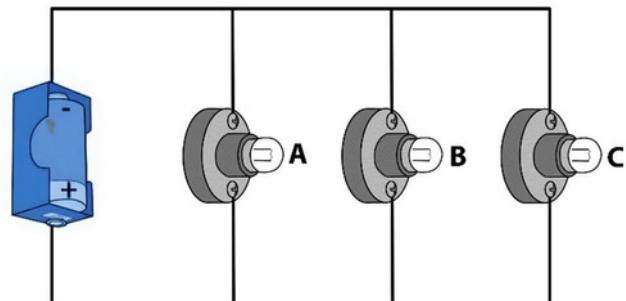


Electrical Circuits - Exercise 1

Upper Primary Advance Science

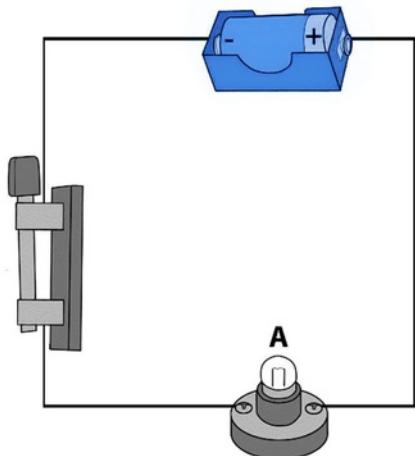Determine if the bulb will light up or not. Put a cross (X) if it does not light up and a tick if it does (✓).



Electrical Circuits - Exercise 1 - Solutions

Upper Primary Advance Science

Determine if the bulb will light up or not. Put a cross (X) if it does not light up and a tick if it does (✓).

