
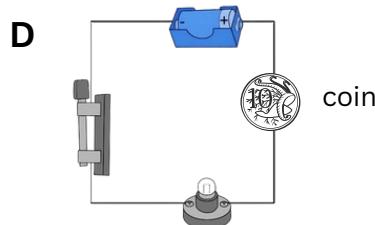
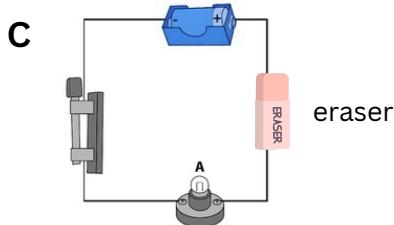
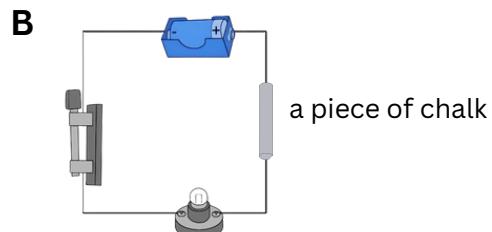


Electrical Circuits - Exercise 2

Upper Primary Advance Science

Choose the correct answers and circle your option.

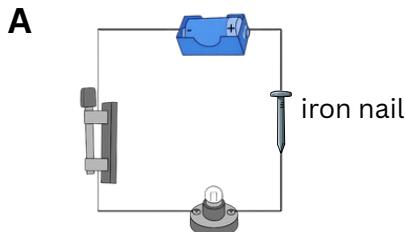1. Which of the following bulbs will light up? (Hint: Choose 2)



2. The diagram below shows a battery. Which part of the battery should the metal tip of the light bulb be connected to?



3. A _____ is used to open or close a circuit.

- A. gap
- B. path
- C. plug
- D. switch

4. The torch uses electricity from the

- A. sun**
- B. bulb**
- C. battery**
- D. power station**

5. Which of the following statements about electricity is **incorrect**?





- A. It is a kind of energy.
- B. It is used to light up bulbs.
- C. It can flow through a closed circuit.
- D. It can be seen because it produces light.

Electrical Circuits - Exercise 2 - Solutions

Upper Primary Advance Science

Choose the correct answers and circle your option.

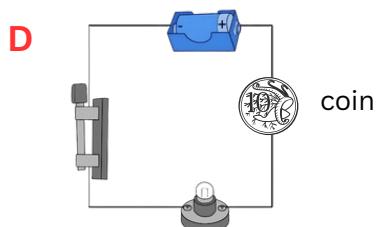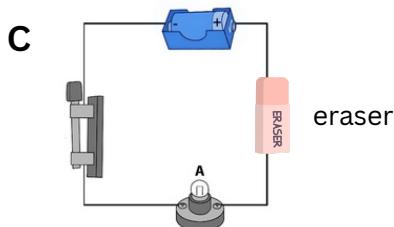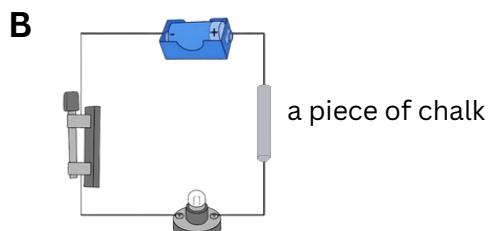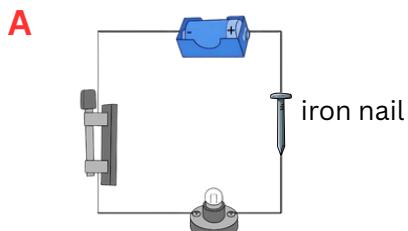1. Which of the following bulbs will light up? (Hint: Choose 2)



2. The diagram below shows a battery. Which part of the battery should the metal tip of the light bulb be connected to?



3. A _____ is used to open or close a circuit.

- A. gap
- B. path
- C. plug
- D. switch

4. The torch uses electricity from the

- A. sun
- B. bulb
- C. battery
- D. power station

5. Which of the following statements about electricity is **incorrect**?

- A. It is a kind of energy.
- B. It is used to light up bulbs.
- C. It can flow through a closed circuit.
- D. It can be seen because it produces light.