

Label the Electrical Circuit

Middle Primary Advance Science



Label the parts of the electrical circuit.

switch

battery

wire

bulb

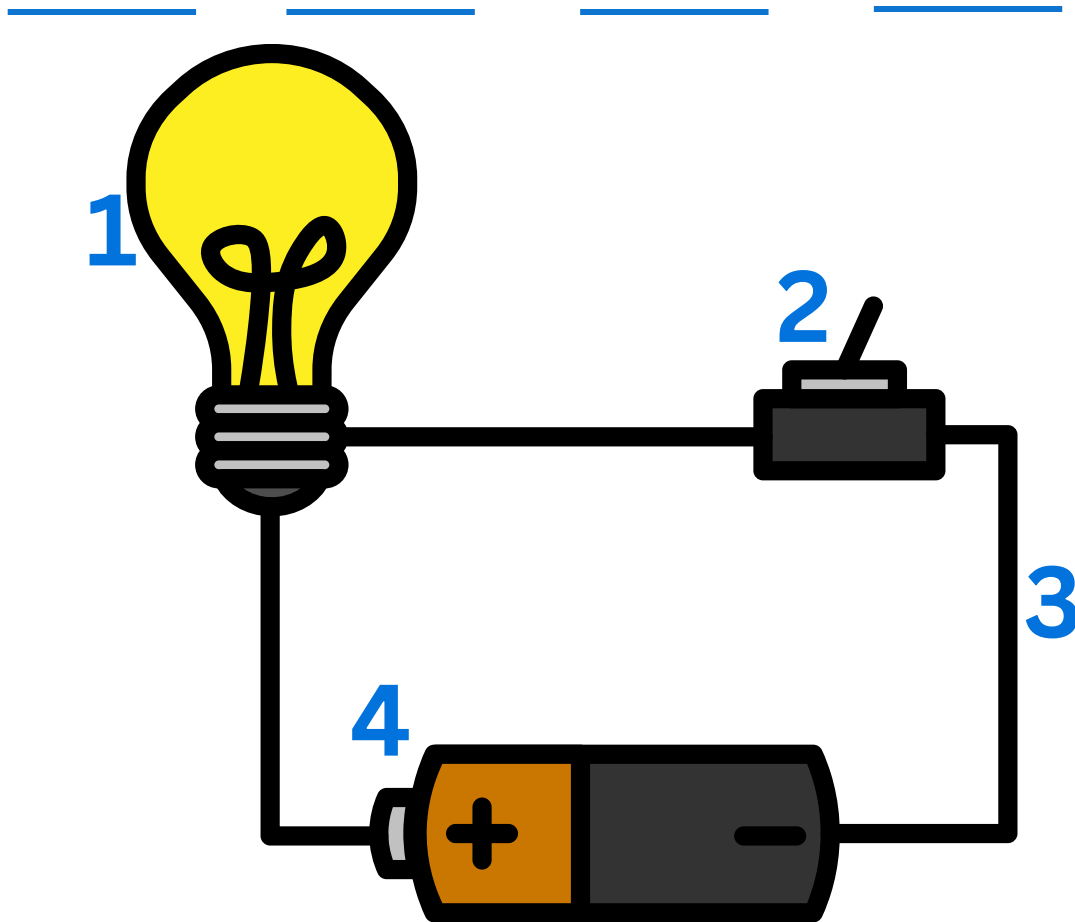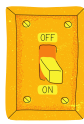

- 1 _____
- 2 _____
- 3 _____
- 4 _____

Label the Electrical Circuit - Solutions

Middle Primary Advance Science

Label the parts of the electrical circuit.

switch


battery

wire

bulb



bulb

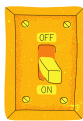


switch



battery



wire

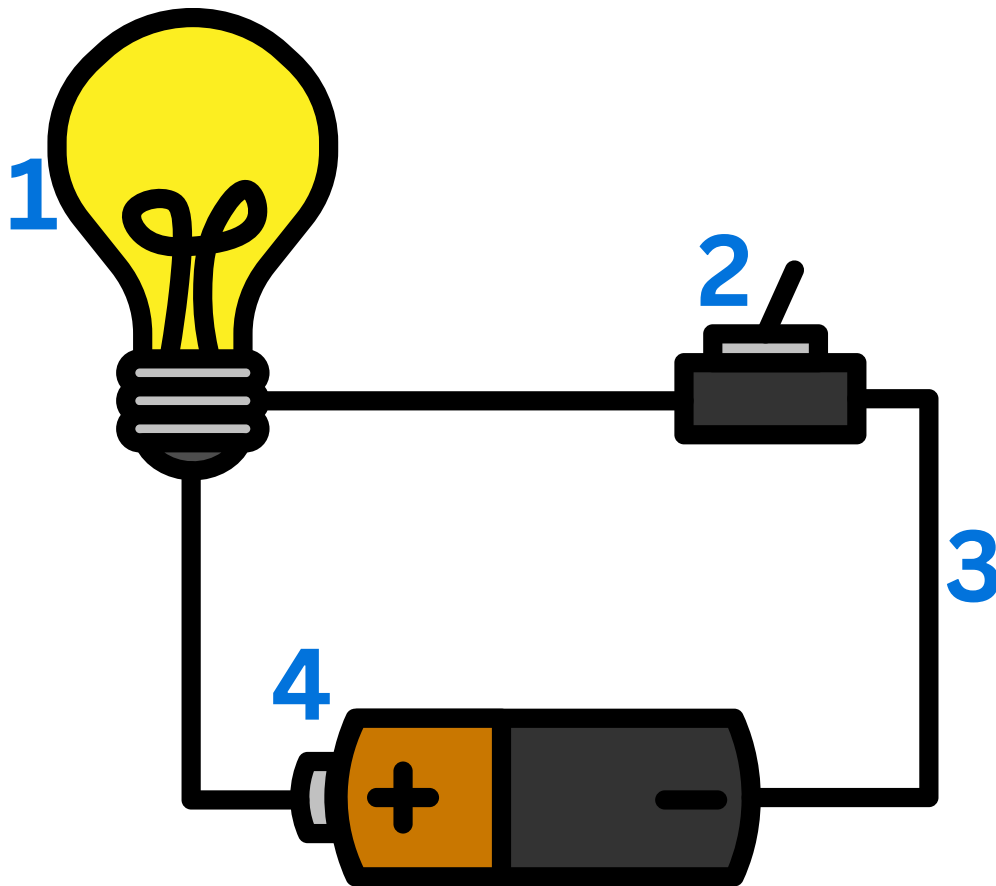

- 1 bulb
- 2 switch
- 3 wire
- 4 battery