

Will it Light Up?

Upper Primary Beginner Science


Explain why each bulb will not light up.




Will it Light Up? - Solutions

Upper Primary Beginner Science


Explain why each bulb will not light up.

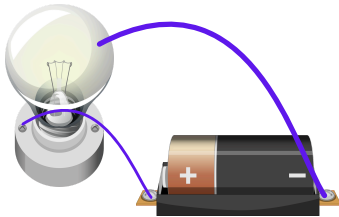

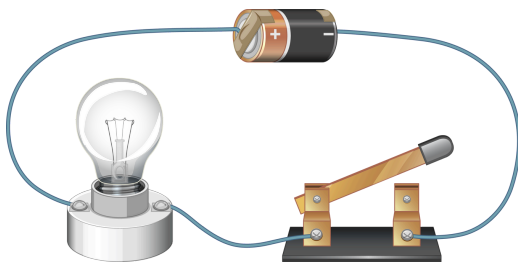
One wire is connected to the bulb instead of the metal connector.



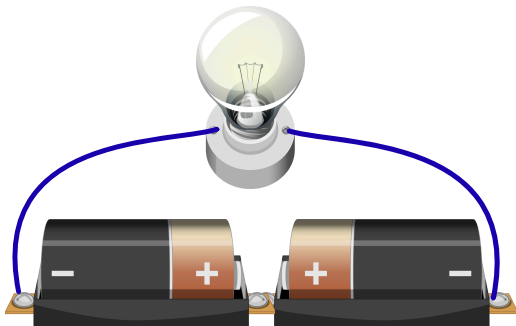The switch is open, so there is not a complete circuit.



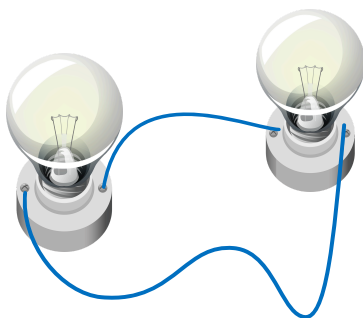One of the batteries needs to be switched around.



There is no power source.